

# Introduction to Electrical Circuits

**Final Term  
Lecture - 02**

Reference Book:

**Introductory Circuit Analysis**

Robert L. Boylestad, 11<sup>th</sup> Edition



**Faculty of Engineering**

**American International University-Bangladesh**





| Week No. | Class No. | Chapter No. | Article No. , Name and Contents                                     | Example No.     |
|----------|-----------|-------------|---|-----------------|
| W8       | FC1       | Chapter 15  | 15.2 IMPEDANCE AND THE PHASOR DIAGRAM<br>Resistive Elements         | 15.1-15.6       |
|          |           | Chapter 15  | 15.3 SERIES CONFIGURATION (RL, RC, and RLC) with power distribution | 15.8            |
|          |           |             | 15.4 VOLTAGE DIVIDER RULE   | 15.9,<br>15.11  |
|          | FC2       | Chapter 15  | 15.7 ADMITTANCE AND SUSCEPTANCE                                     | 15.13,<br>15.14 |
|          |           |             | 15.8 PARALLEL ac NETWORKS (RL, RC and RLC) with power distribution  |                 |
|          |           |             | 15.9 CURRENT DIVIDER RULE   | 15.16,<br>15.17 |



# Pure Capacitive Circuit


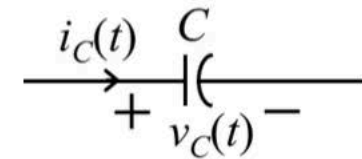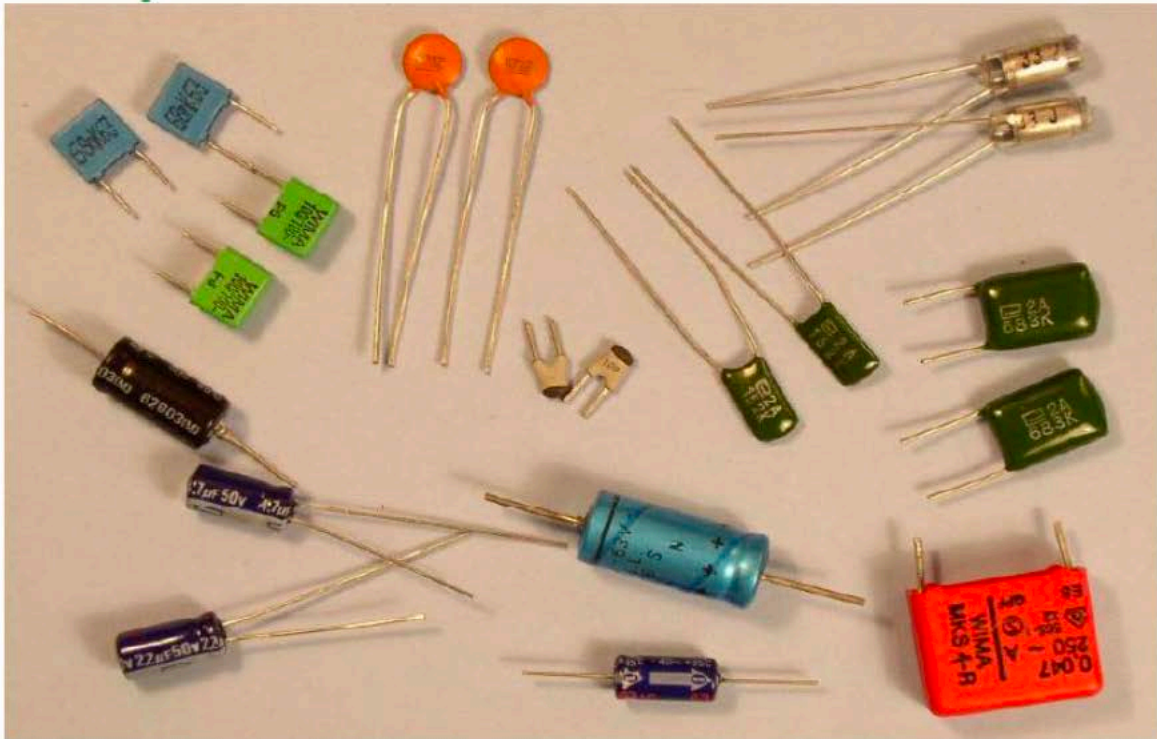
## Response of Basic Capacitor or Condenser Element to a Sinusoidal Voltage or Current



**Voltage and current relation in a capacitor:**

$$v_C(t) = \frac{1}{C} \int i_C(t) dt$$

$$i_C(t) = C \frac{dv_C(t)}{dt}$$



Let, the input is  $v(t) = V_m \sin \omega t$  V, according to KVL, we have:  $v(t) = v_C(t) = V_m \sin \omega t$

For a capacitance the relation of voltage and current is:

$$i(t) = i_C(t) = C \frac{dv_C(t)}{dt} = CV_m \frac{d(\sin \omega t)}{dt} = \omega C V_m \cos \omega t$$

$$i(t) = \omega C V_m \sin(\omega t + 90^\circ) = I_m \sin(\omega t + \theta_i)$$

**Magnitude of impedance,  $Z = \frac{V_m}{I_m} = \frac{1}{\omega C} = X_C \quad \Omega$**

**Capacitive reactance,  $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad \Omega$**




**Angle of current,  $\theta_i = 90^\circ$**

**Angle of impedance,  $\theta_Z = \theta_v - \theta_i = -90^\circ$**

Impedance of a Capacitor,  $Z = Z_C = X_C \angle -90^\circ = -j X_C \Omega$

The phase difference between voltage across and current through a capacitor is  $90^\circ$ .

For a purely capacitive element, the voltage lags the current through the capacitive element by  $90^\circ$ . Or, the current leads the voltage in a capacitive element by  $90^\circ$ .

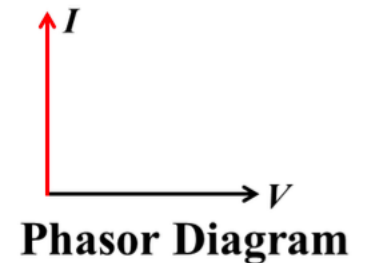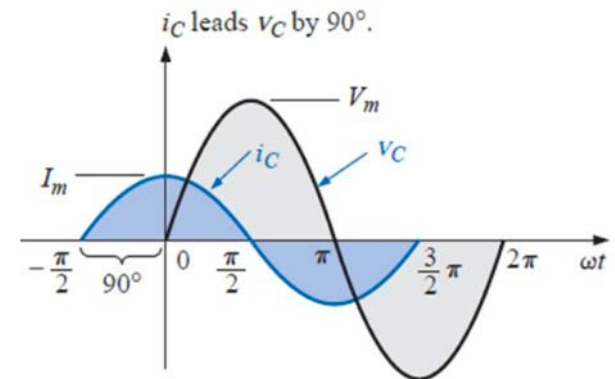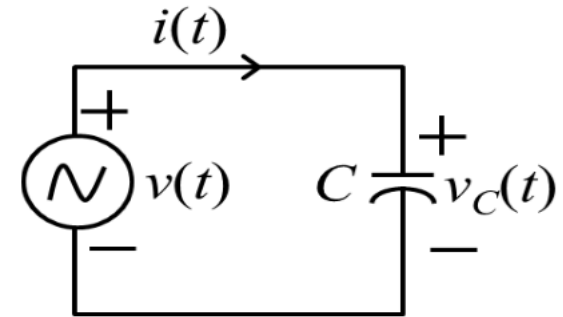

**EXAMPLE 15.5** Using complex algebra,

- Find the current  $i_C$  for the circuit in Fig. 15.15.
- Sketch the  $v_C$  and  $i_C$  curves.


**Solution:**

- $v_C = 15 \sin \omega t \Rightarrow$  phasor notation  $\mathbf{V} = 10.605 \text{ V } \angle 0^\circ$


$$\mathbf{I}_C = \frac{\mathbf{V}_C}{\mathbf{Z}_C} = \frac{V \angle \theta}{X_C \angle -90^\circ} = \frac{10.605 \text{ V } \angle 0^\circ}{2 \Omega \angle -90^\circ} = 5.303 \text{ A } \angle 90^\circ$$

and  $i_C = \sqrt{2}(5.303) \sin(\omega t + 90^\circ) = 7.5 \sin(\omega t + 90^\circ)$

- Note Fig. 15.16.

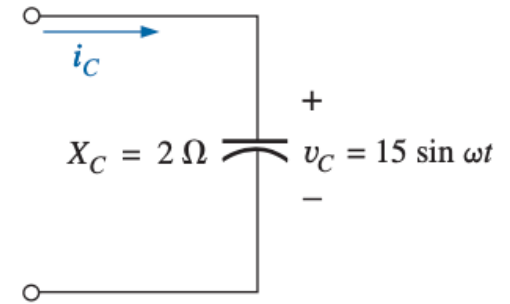


**FIG. 15.15**  
Example 15.5.

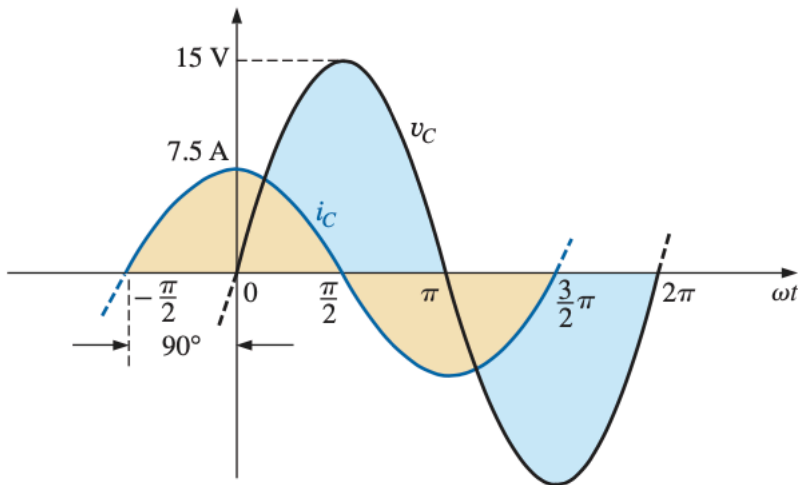

**FIG. 15.16**

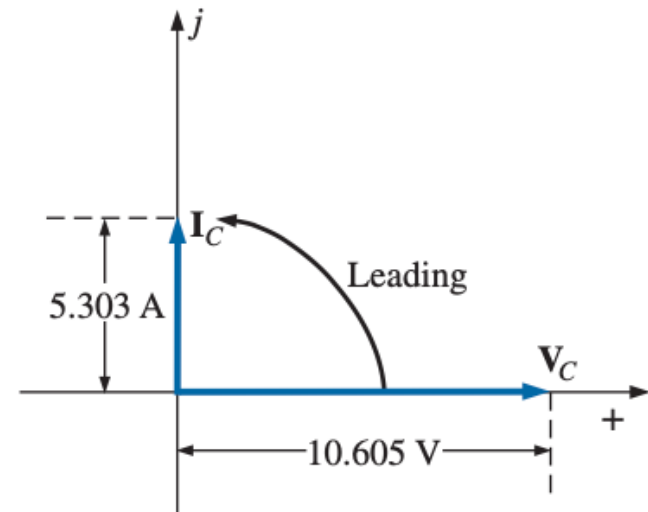Waveforms for Example 15.5.




**EXAMPLE 15.6** Using complex algebra,


- Find the voltage  $v_C$  for the circuit in Fig. 15.17.
- Sketch the  $v_C$  and  $i_C$  curves.

**Solution:**


- $i_C = 6 \sin(\omega t - 60^\circ) \Rightarrow$  phasor notation  $\mathbf{I}_C = 4.242 \text{ A} \angle -60^\circ$   
 $\mathbf{V}_C = \mathbf{I}\mathbf{Z}_C = (I \angle \theta)(X_C \angle -90^\circ) = (4.242 \text{ A} \angle -60^\circ)(0.5 \Omega \angle -90^\circ)$   
 $= 2.121 \text{ V} \angle -150^\circ$   
and  $v_C = \sqrt{2}(2.121) \sin(\omega t - 150^\circ) = 3.0 \sin(\omega t - 150^\circ)$
- Note Fig. 15.18.

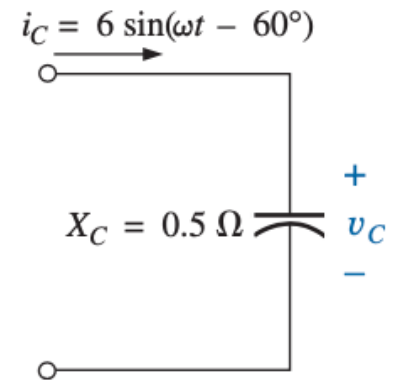

**FIG. 15.17**  
Example 15.6.

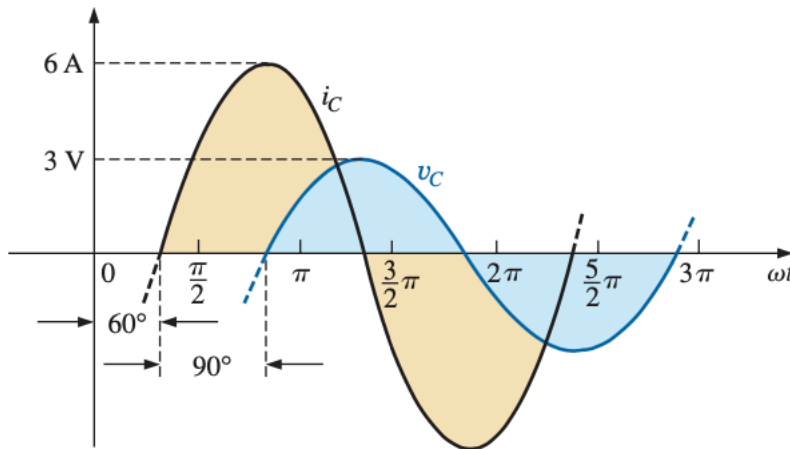

**FIG. 15.18**  
Waveforms for Example 15.6.

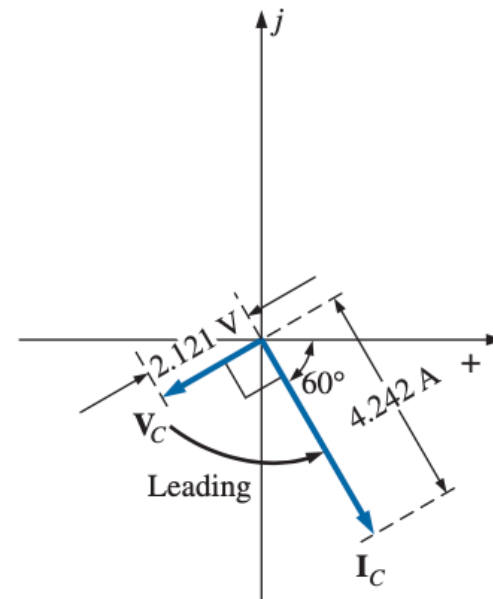

## Summary For a pure Capacitive Load

Magnitude of impedance,  $Z = \frac{V_m}{I_m} = X_C \quad \Omega$        $\theta_i = \theta_v + 90^\circ$        $\theta_v = \theta_i - 90^\circ$

Angle of impedance,  $\theta_z = \theta_v - \theta_i = -90^\circ$

Impedance of a Capacitor,  $Z = Z_C = X_C \angle -90^\circ = -jX_C \quad \Omega$

The phase difference between voltage across and current through a capacitor is  $90^\circ$ .

*The voltage lags the current in an inductor by  $90^\circ$ .*

*The current leads the voltage in an inductor by  $90^\circ$ .*

The power factor is 0 which is called **zero leading power factor**.

The reactive factor is -1.

The active power is 0 that means **zero**.

The apparent power equals to reactive power.

Capacitor supply the reactive power.





|  | Resistance                              | Inductance   | Capacitance   |
|--|---|--|---|
| Magnitude of impedance( $Z$ ) [ $\Omega$ ]   | $R$                                     | $X_L$  | $X_C$   |
| Angle of impedance( $\theta=\theta_z$ )      | $0^\circ$                               | $90^\circ$   | $-90^\circ$   |
| Impedance ( $Z$ ) [ $\Omega$ ]               | $Z_R=R\angle 0^\circ=R+j0$              | $Z_L=X_L\angle 90^\circ=0+jX_L$                      | $Z_C=X_C\angle -90^\circ=0-jX_L$                      |
| Phase difference between voltage and current | $0^\circ$                               | $90^\circ$   | $-90^\circ$   |
| Relation between voltage and current         | Voltage and current are in phase        | Voltage leads current<br>Current <b>lags</b> voltage | Voltage lags current<br>Currents <b>leads</b> voltage |
| Power factor ( $pf=\cos\theta$ )             | Unity (1)                               | Zero <b>lagging</b> power factor ( $pf=0$ )          | Zero <b>leading</b> power factor ( $pf=0$ )           |
| Reactive factor ( $rf=\sin\theta$ )          | 0                                       | 1  | -1  |
| Power ( $P$ ) [W]                            | $V_{rms}I_{rms}=I_{rms}^2R=V_{rms}^2/R$ | 0  | 0   |
| Reactive power ( $Q=P_x$ ) [Var]             | 0                                       | $V_{rms}I_{rms}=I_{rms}^2X_L$<br>$=V_{rms}^2/X_L$    | $-V_{rms}I_{rms}=-I_{rms}^2X_C$<br>$=-V_{rms}^2/X_C$  |
| Apparent power ( $S$ ) [VA]                  | $S=V_{rms}I_{rms}$                      | $S=V_{rms}I_{rms}$                                   | $S=V_{rms}I_{rms}$                                    |




# Impedance Diagram

For any network,

- the resistance will *always* appear on the positive real axis,
- the inductive reactance on the positive imaginary axis, and
- the capacitive reactance on the negative imaginary axis.

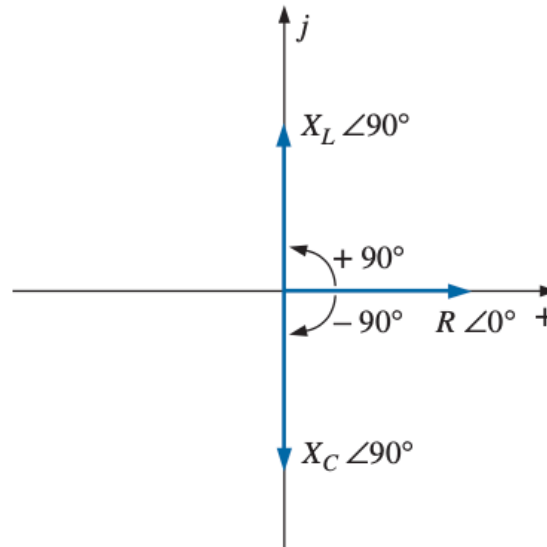
The result is an **impedance diagram** that can reflect the individual and total impedance levels of an ac network.



# Series Configuration

- The overall properties of series ac circuits (Fig. 15.23) are the same as those for dc circuits.
- For instance, the total impedance of a system is the sum of the individual impedances and the current  $\mathbf{I}$  is the same through each impedance.

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3 + \cdots + \mathbf{Z}_N$$

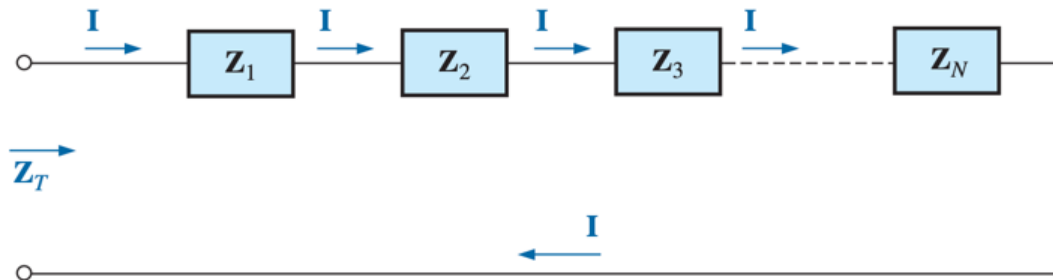


**FIG. 15.23**  
*Series impedances.*




**EXAMPLE 15.9** Draw the impedance diagram for the circuit in Fig. 15.24, and find the total impedance.

**Solution:** As indicated by Fig. 15.25, the input impedance can be found graphically from the impedance diagram by properly scaling the real and imaginary axes and finding the length of the resultant vector  $Z_T$  and angle  $\theta_T$ . Or, by using vector algebra, we obtain

$$\begin{aligned} Z_T &= Z_1 + Z_2 \\ &= R \angle 0^\circ + X_L \angle 90^\circ \\ &= R + jX_L = 4 \Omega + j 8 \Omega \\ Z_T &= 8.94 \Omega \angle 63.43^\circ \end{aligned}$$

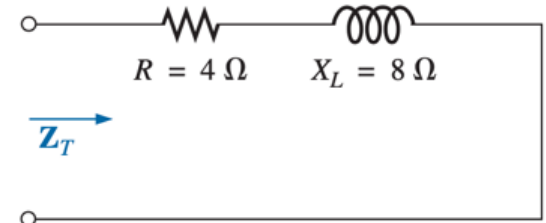

**FIG. 15.24**  
Example 15.9.

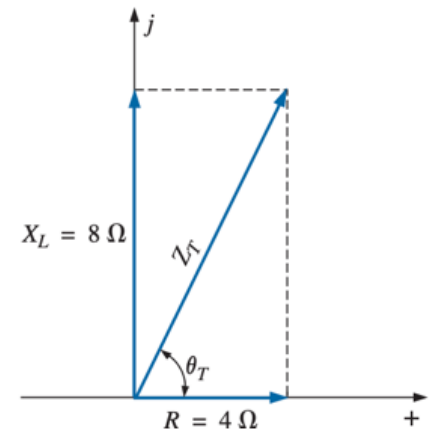


**FIG. 15.25**  
Impedance diagram for Example 15.9.




**EXAMPLE 15.10** Determine the input impedance to the series network in Fig. 15.26. Draw the impedance diagram.

**Solution:**

$$\begin{aligned}
 \mathbf{Z}_T &= \mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3 \\
 &= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\
 &= R + jX_L - jX_C \\
 &= R + j(X_L - X_C) = 6 \, \Omega + j(10 \, \Omega - 12 \, \Omega) = 6 \, \Omega - j2 \, \Omega \\
 \mathbf{Z}_T &= 6.32 \, \Omega \angle -18.43^\circ
 \end{aligned}$$

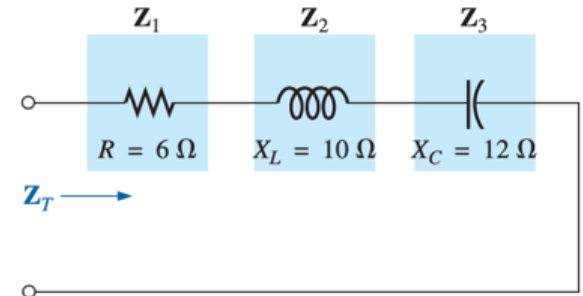

**FIG. 15.26**  
Example 15.10

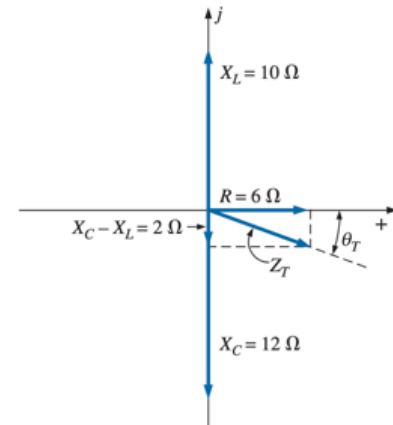

**FIG. 15.27**  
Impedance diagram for Example 15.10.

# Resistance and Inductance Series Circuit





**Faculty of Engineering**

**American International University-Bangladesh**
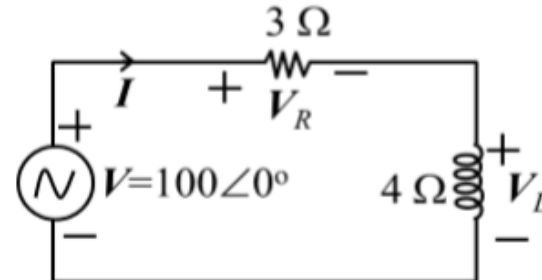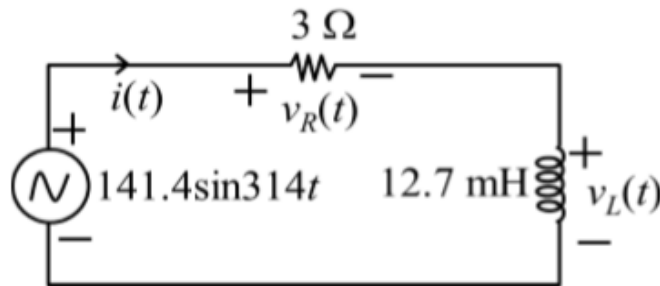
### Example

A voltage  $141.4\sin 314t$  V is applied to a  $RL$  series circuit which consists  $R=3$  ohms,  $L = 12.7$  mH. (a) Draw the circuit diagram. (b) Calculate (i) the inductive reactance, (ii) the impedance, (iii) the current, (iv) the voltage drop across the resistance and inductance, (v) the power factor and reactive factor, (vi) the power, reactive power, apparent power. (vi) Verify the KVL. (c) Write the instantaneous expression of current, voltage drop across the resistance, voltage drop across the inductance. (d) Draw the impedance diagram, phasor diagram, and power triangle.

**Solution:**  $X_L = \omega L = 314 \times 0.0127 = 4 \Omega$        $V = \frac{V_m}{\sqrt{2}} \angle \theta_v = \frac{141.4}{\sqrt{2}} \angle 0^\circ = 100 \angle 0^\circ \text{ V}$   
 $Z_L = jX_L = j4 = 4 \angle 90^\circ \Omega$        $Z_R = 3 = 3 \angle 0^\circ \Omega$



$$Z = Z_{RL} = 3 + j4 = 5\angle 53.13^\circ \quad \Omega \quad V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 100 \text{ V} \quad V = 100\angle 0^\circ \text{ V}$$

**Current:**  $I = \frac{V}{Z} = \frac{100\angle 0^\circ}{5\angle 53.13^\circ} = 20\angle -53.13^\circ \text{ A}$

**Voltage drop across the resistance:**  $V_R = IZ_R = (20\angle -53.13^\circ)(3\angle 0^\circ) = 60\angle -53.13^\circ \text{ V}$

**Voltage drop across the inductance:**  $V_L = IZ_L = (20\angle -53.13^\circ)(4\angle 90^\circ) = 80\angle 36.87^\circ \text{ V}$

**Verification of KVL:**  $V = V_R + V_L = 60\angle -53.13^\circ + 80\angle 36.87^\circ \text{ V}$

$$V = 36 - j48 + 64 + j48 = 100 \text{ V (equal to supply voltage)}$$

**Angle of impedance,  $\theta = \theta_z = \theta_v - \theta_i = 53.13^\circ$**

**Power Factor :**  $\text{pf} = \cos(\theta_z) = \cos[53.13^\circ] = 0.6 \text{ lagging}$

**Reactive Factor :**  $\text{rf} = \sin(\theta_z) = \sin[53.13^\circ] = 0.8$








**Power or Active Power :**  $P = VI \cos \theta_z = 100 \times 20 \times 0.6 = 1200 \text{ W}$

$$P = I^2 R = 20^2 \times 3 = 1200 \text{ W} \quad P = \frac{V_R^2}{R} = \frac{60^2}{3} = 1200 \text{ W}$$

**Reactive Power :**  $Q_L = VI \sin \theta_z = 100 \times 20 \times 0.8 = 1600 \text{ Var}$

$$Q_L = I^2 X_L = 20^2 \times 4 = 1600 \text{ Var} \quad Q_L = \frac{V_L^2}{X_L} = \frac{80^2}{4} = 1600 \text{ Var}$$

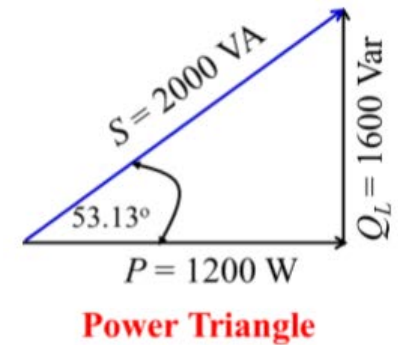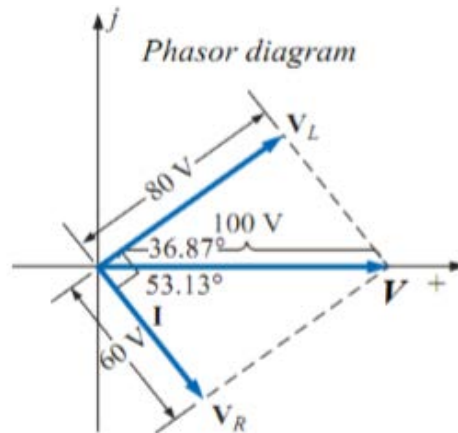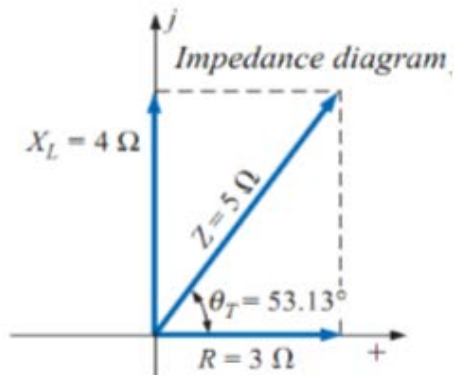**Apparent Power :**  $S = VI = 100 \times 20 = 2000 \text{ VA}$



# Resistance and Capacitance Series Circuit



**Faculty of Engineering**



**American International University-Bangladesh**

### Example

A voltage  $141.4\sin 314t$  V is applied to a  $RC$  series circuit which consists  $R=3$  ohms,  $C=796.18 \mu\text{F}$ . (a) Draw the circuit diagram. (b) Calculate (i) the capacitive reactance, (ii) the impedance, (iii) the current, (iv) the voltage drop across the resistance and capacitance, (v) the power factor and reactive factor, (vi) the power, reactive power, apparent power. (vi) Verify the KVL. (c) Write the instantaneous expression of current, voltage drop across the resistance, voltage drop across the capacitance. (d) Draw the impedance diagram, phasor diagram, and power triangle.

**Solution:** Capacitive reactance:  $X_C = \frac{1}{\omega C} = \frac{1}{314 \times 796.18 \times 10^{-6}} = 4 \Omega$
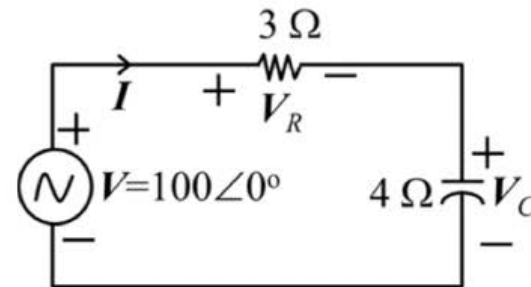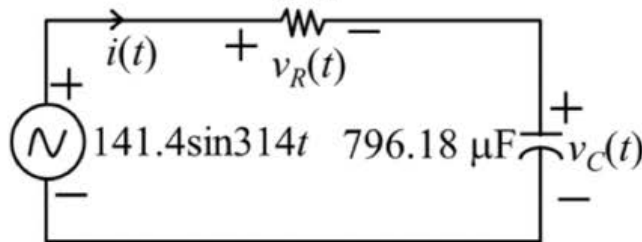
$$V = \frac{V_m}{\sqrt{2}} \angle \theta_v = \frac{141.4}{\sqrt{2}} \angle 0^\circ = 100 \angle 0^\circ \text{ V}$$



$$Z_C = -jX_C = -j4 = 4\angle -90^\circ \Omega \quad Z_R = 3 = 3\angle 0^\circ \Omega$$

$$Z = Z_{RC} = 3 - j4 = 5\angle -53.13^\circ \Omega$$

**Current:**  $I = \frac{V}{Z} = \frac{100\angle 0^\circ}{5\angle -53.13^\circ} = 20\angle 53.13^\circ \text{ A}$

**Voltage drop across the resistance:**  $V_R = IZ_R = (20\angle 53.13^\circ)(3\angle 0^\circ) = 60\angle 53.13^\circ \text{ V}$

**Voltage drop across the inductance:**  $V_C = IZ_C = (20\angle 53.13^\circ)(4\angle -90^\circ) = 80\angle -36.87^\circ \text{ V}$

**Verification of KVL:**  $V = V_R + V_C = 60\angle 53.13^\circ + 80\angle -36.87^\circ \text{ V}$

$$V = 36 + j48 + 64 - j48 = 100 \text{ V (equal to supply voltage)}$$

**Angle of impedance,  $\theta = \theta_z = \theta_v - \theta_i = -53.13^\circ$**

**Power Factor :**  $\text{pf} = \cos(\theta_z) = \cos[-53.13^\circ] = 0.6 \text{ leading}$

**Reactive Factor :**  $\text{rf} = \sin(\theta_z) = \sin[-53.13^\circ] = -0.8$




**Power or Active Power :**  $P = VI \cos \theta_z = 100 \times 20 \times 0.6 = 1200 \text{ W}$

$$P = I^2 R = 20^2 \times 3 = 1200 \text{ W} \quad P = \frac{V_R^2}{R} = \frac{60^2}{3} = 1200 \text{ W}$$


**Reactive Power :**  $Q_L = VI \sin \theta_z = 100 \times 20 \times -0.8 = -1600 \text{ Var}$

$$Q_L = -I^2 X_C = -20^2 \times 4 = -1600 \text{ Var} \quad Q_C = -\frac{V_C^2}{X_C} = -\frac{80^2}{4} = -1600 \text{ Var}$$

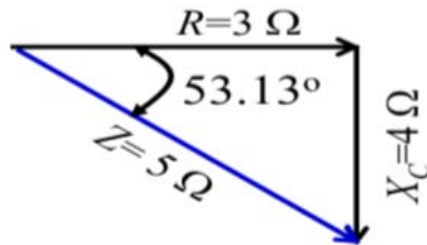
**Apparent Power :**  $S = VI = 100 \times 20 = 2000 \text{ VA}$



**Impedance Diagram**

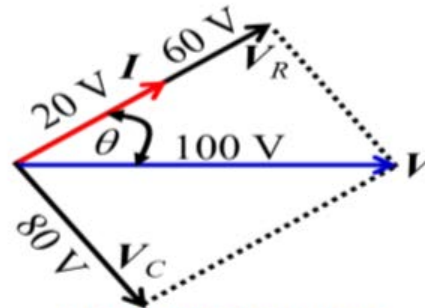

**Phasor Diagram**

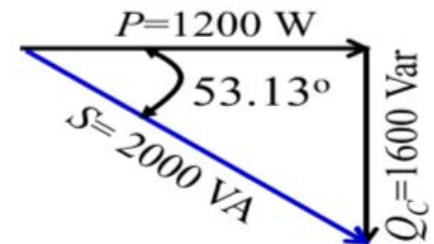

**Power Triangle**



# Resistance, Inductance and Capacitance Series Circuit



**Faculty of Engineering**

**American International University-Bangladesh**

### Example


If  $R=20$  ohms,  $L=0.056$  Henry,  $C = 50 \mu\text{F}$  and applied voltage  $200\sin 377t$ , (a) Draw the circuit diagram. (b) Calculate (i) the capacitive reactance, (ii) the impedance, (iii) the current, (iv) the voltage drop across the resistance and capacitance, (v) the power factor and reactive factor, (vi) the power, reactive power, apparent power. (vi) Verify the KVL. (c) Write the instantaneous expression of current, voltage drop across the resistance, voltage drop across the capacitance. (d) Draw the impedance diagram, phasor diagram, and power triangle.

**Solution:**  $V_m = 200 \text{ V}$     $\omega = 377 \text{ rad/s}$     $R = 20 \Omega$     $L = 0.056 \text{ H}$     $C = 50 \times 10^{-6} \text{ F}$

**Inductive reactance:**  $X_L = \omega L = 377 \times 0.056 = 21.1 \Omega$

**Capacitive reactance:**  $X_C = \frac{1}{\omega C}$
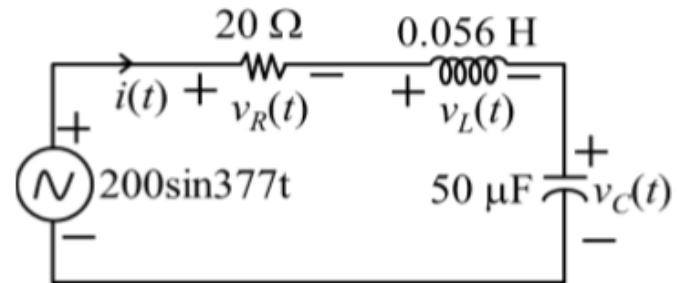
$$= \frac{1}{377 \times 50 \times 10^{-6}} = 53 \Omega$$



$$\mathbf{Z}_R = 20 \angle 0^\circ = 20 \, \Omega \quad \mathbf{Z}_L = 21.1 \angle 90^\circ = j21.1 \, \Omega \quad \mathbf{Z}_C = 53 \angle -90^\circ = -j53 \, \Omega$$

$$\mathbf{Z} = \mathbf{Z}_R + \mathbf{Z}_L + \mathbf{Z}_C = 20 \angle 0^\circ + 21.1 \angle 90^\circ + 53 \angle -90^\circ = 20 + j21.1 - j53 \, \Omega$$

$$\mathbf{Z} = 20 - j31.9 = 37.65 \angle -57.9^\circ \, \Omega$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{200}{\sqrt{2}} = 141.4 \, \text{V}$$


$$\mathbf{V} = 141.4 \angle 0^\circ \, \text{V}$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{141.4 \angle 0^\circ}{37.56 \angle -57.9^\circ} = 3.76 \angle 57.9^\circ = 2 + j3.2 \, \text{A}$$

$$\mathbf{V}_R = \mathbf{I}\mathbf{Z}_R = (3.76 \angle 57.9^\circ)(20 \angle 0^\circ) = 75.1 \angle 57.9^\circ = 40 + j63.64 \, \text{V}$$

$$\mathbf{V}_L = \mathbf{I}\mathbf{Z}_L = (3.76 \angle 57.9^\circ)(21.1 \angle 90^\circ) = 79.24 \angle 148^\circ = -67 + j42.1 \, \text{V}$$
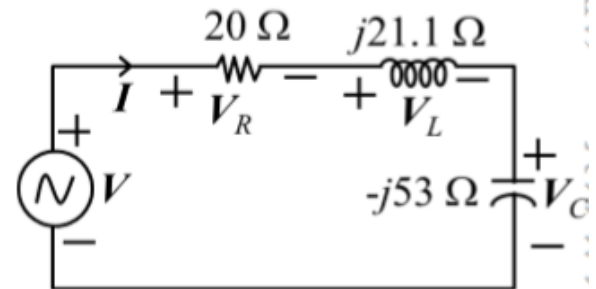
$$\mathbf{V}_C = \mathbf{I}\mathbf{Z}_C = (3.76 \angle 57.9^\circ)(53 \angle -90^\circ) = 199 \angle -32.1^\circ = 169 - j106 \, \text{V}$$



### Verification of KVL:

$$\mathbf{V} = 40 + j63.64 - 67 + j42.1 + 169 - j106 = 141.4 \, \text{V (equal to supply voltage)}$$








$$\theta = \theta_z = \theta_v - \theta_i = -57.9^\circ \quad pf = \cos \theta = \cos(-57.9^\circ) = 0.53$$

$$rf = \sin \theta = \sin(-57.9^\circ) = -0.85$$

$$S = VI = 141.4 \times 3.76 = 531 \text{ VA} \quad P = VI \cos \theta_z = 141.4 \times 3.76 \times 0.53 = 282.1 \text{ W}$$

$$Q = Q_L - Q_C = VI \sin \theta_z = 141.4 \times 3.76 \times -0.85 = -500 \text{ Var}$$
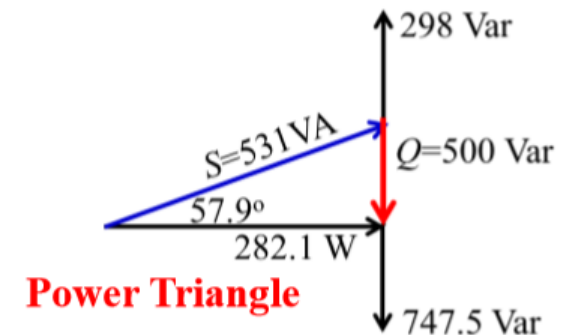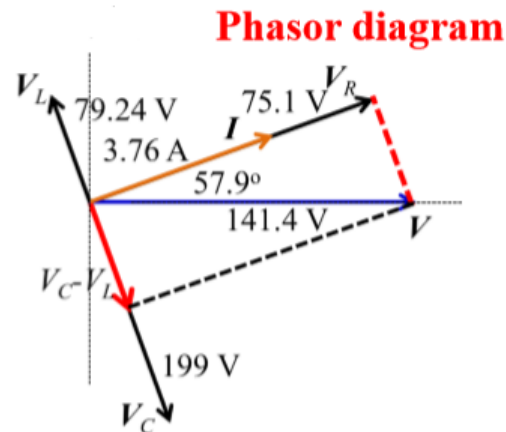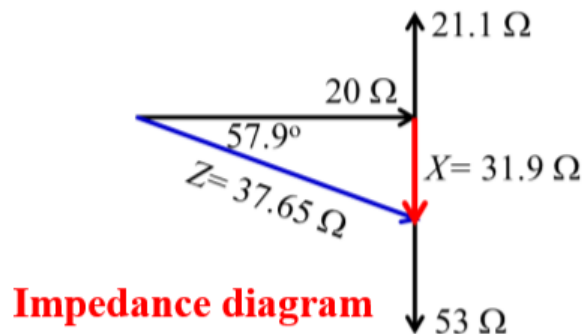
$$Q_L = I^2 X_L = 3.76^2 \times 21.1 = 298 \text{ Var} \quad Q_C = -I^2 X_C = -3.76^2 \times 53 = -747.5 \text{ Var}$$



|   | <i>RL</i> series Circuit  | <i>RC</i> series Circuit   | <i>RLC</i> series Circuit                               |
|---|---|--|---|
| Magnitude of impedance( <i>Z</i> ) [ $\Omega$ ] | $Z = \sqrt{R^2 + X_L^2}$  | $Z = \sqrt{R^2 + X_C^2}$   | $Z = \sqrt{R^2 + (X_L - X_C)^2}$                        |
| Angle of impedance( $\theta = \theta_z$ )       | $\theta = \tan^{-1} \left[ \frac{X_L}{R} \right]$                     | $\theta = -\tan^{-1} \left[ \frac{X_C}{R} \right]$                     | $\theta = \tan^{-1} \left[ \frac{X_L - X_C}{R} \right]$ |
| Impedance ( <i>Z</i> ) [ $\Omega$ ]             | $Z = Z \angle \theta = R + jX_L$                                      | $Z = Z \angle \theta = R - jX_C$                                       | $Z = Z \angle \theta = R + j(X_L - X_C)$                |
| Phase difference between voltage and current    | $\theta = \theta_v - \theta_i > 0$<br>Between $0^\circ$ to $90^\circ$ | $\theta = \theta_v - \theta_i < 0$<br>Between $-90^\circ$ to $0^\circ$ | Depends on the value of $X_L$ and $X_C$                 |
| Relation between voltage and current            | Voltage leads current<br>i.e.<br>Current lags voltage                 | Voltage lags current<br>i.e.<br>Current leads voltage                  | Depends on the value of $X_L$ and $X_C$                 |



# Voltage Divider Rule

The voltage ( $V_x$ ) across one or more elements in series that have total impedance  $Z_x$ , can be given by:

$$V_x = \frac{Z_x}{Z_T} E = \frac{Z_x}{Z_T} V$$

where,  $E$  or  $V$  is the total voltage appearing across the series circuit, and  $Z_T$  is the total impedance of the series circuit.




**EXAMPLE 15.11** Using the voltage divider rule, find the voltage across each element of the circuit in Fig. 15.43.

**Solution:**

$$\begin{aligned} V_C &= \frac{\mathbf{Z}_C \mathbf{E}}{\mathbf{Z}_C + \mathbf{Z}_R} = \frac{(4 \Omega \angle -90^\circ)(100 \text{ V} \angle 0^\circ)}{4 \Omega \angle -90^\circ + 3 \Omega \angle 0^\circ} = \frac{400 \text{ V} \angle -90^\circ}{3 - j4} \\ &= \frac{400 \text{ V} \angle -90^\circ}{5 \angle -53.13^\circ} = \mathbf{80 \text{ V} \angle -36.87^\circ} \end{aligned}$$

$$\begin{aligned} V_R &= \frac{\mathbf{Z}_R \mathbf{E}}{\mathbf{Z}_C + \mathbf{Z}_R} = \frac{(3 \Omega \angle 0^\circ)(100 \text{ V} \angle 0^\circ)}{5 \Omega \angle -53.13^\circ} = \frac{300 \text{ V} \angle 0^\circ}{5 \angle -53.13^\circ} \\ &= \mathbf{60 \text{ V} \angle +53.13^\circ} \end{aligned}$$

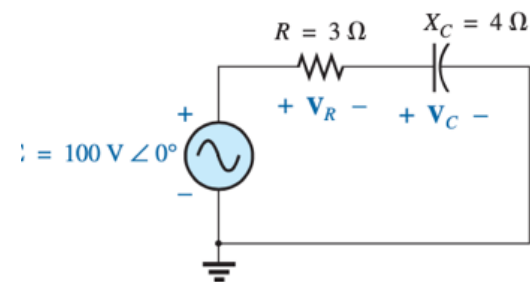


**FIG. 15.43**  
Example 15.11.



**EXAMPLE 15.13** For the circuit in Fig. 15.46,

- Calculate  $\mathbf{I}$ ,  $\mathbf{V}_R$ ,  $\mathbf{V}_L$ , and  $\mathbf{V}_C$  in phasor form.
- Calculate the total power factor.
- Calculate the average power delivered to the circuit.
- Draw the phasor diagram.
- Obtain the phasor sum of  $\mathbf{V}_R$ ,  $\mathbf{V}_L$ , and  $\mathbf{V}_C$ , and show that it equals the input voltage  $\mathbf{E}$ .
- Find  $\mathbf{V}_R$  and  $\mathbf{V}_C$  using the voltage divider rule.

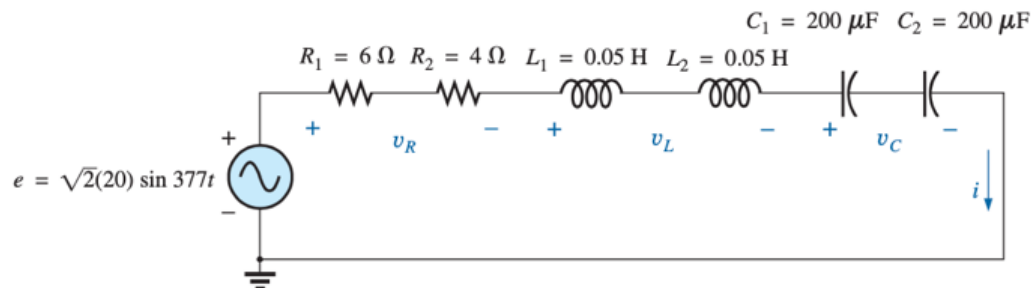

**FIG. 15.46**  
Example 15.13.



### Solutions:

- a. Combining common elements and finding the reactance of the inductor and capacitor, we obtain

$$R_T = 6\ \Omega + 4\ \Omega = 10\ \Omega$$


$$L_T = 0.05\ \text{H} + 0.05\ \text{H} = 0.1\ \text{H}$$

$$C_T = \frac{200\ \mu\text{F}}{2} = 100\ \mu\text{F}$$

$$X_L = \omega L = (377\ \text{rad/s})(0.1\ \text{H}) = 37.70\ \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(377\ \text{rad/s})(100 \times 10^{-6}\ \text{F})} = \frac{10^6\ \Omega}{37,700} = 26.53\ \Omega$$

Redrawing the circuit using phasor notation results in Fig. 15.47.

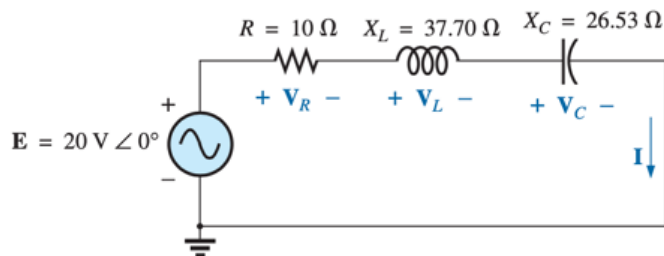

**FIG. 15.47**

Applying phasor notation to the circuit in Fig. 15.46.

For the circuit in Fig. 15.47,

$$\begin{aligned} \mathbf{Z}_T &= R \angle 0^\circ + X_L \angle 90^\circ + X_C \angle -90^\circ \\ &= 10\ \Omega + j 37.70\ \Omega - j 26.53\ \Omega \\ &= 10\ \Omega + j 11.17\ \Omega = \mathbf{15\ \Omega \angle 48.16^\circ} \end{aligned}$$

The current  $\mathbf{I}$  is

$$\mathbf{I} = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{20\ \text{V} \angle 0^\circ}{15\ \Omega \angle 48.16^\circ} = \mathbf{1.33\ \text{A} \angle -48.16^\circ}$$

The voltage across the resistor, inductor, and capacitor can be found using Ohm's law:

$$\begin{aligned} \mathbf{V}_R &= \mathbf{I} \mathbf{Z}_R = (1.33\ \text{A} \angle -48.16^\circ)(10\ \Omega \angle 0^\circ) \\ &= \mathbf{13.30\ \text{V} \angle -48.16^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{V}_L &= \mathbf{I} \mathbf{Z}_L = (1.33\ \text{A} \angle -48.16^\circ)(37.70\ \Omega \angle 90^\circ) \\ &= \mathbf{50.14\ \text{V} \angle 41.84^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{V}_C &= \mathbf{I} \mathbf{Z}_C = (1.33\ \text{A} \angle -48.16^\circ)(26.53\ \Omega \angle -90^\circ) \\ &= \mathbf{35.28\ \text{V} \angle -138.16^\circ} \end{aligned}$$



- b. The total power factor, determined by the angle between the applied voltage  $\mathbf{E}$  and the resulting current  $\mathbf{I}$ , is  $48.16^\circ$ :

$$F_p = \cos \theta = \cos 48.16^\circ = \mathbf{0.667 \text{ lagging}}$$

or 
$$F_p = \cos \theta = \frac{R}{Z_T} = \frac{10 \, \Omega}{15 \, \Omega} = \mathbf{0.667 \text{ lagging}}$$

- c. The total power in watts delivered to the circuit is

$$P_T = EI \cos \theta = (20 \, \text{V})(1.33 \, \text{A})(0.667) = \mathbf{17.74 \, \text{W}}$$

- e. The phasor sum of  $\mathbf{V}_R$ ,  $\mathbf{V}_L$ , and  $\mathbf{V}_C$  is

$$\begin{aligned} \mathbf{E} &= \mathbf{V}_R + \mathbf{V}_L + \mathbf{V}_C \\ &= 13.30 \, \text{V} \angle -48.16^\circ + 50.14 \, \text{V} \angle 41.84^\circ + 35.28 \, \text{V} \angle -138.16^\circ \\ \mathbf{E} &= 13.30 \, \text{V} \angle -48.16^\circ + 14.86 \, \text{V} \angle 41.84^\circ \end{aligned}$$


Therefore,

$$E = \sqrt{(13.30 \, \text{V})^2 + (14.86 \, \text{V})^2} = \mathbf{20 \, \text{V}}$$

and  $\theta_E = \mathbf{0^\circ}$  (from phasor diagram)

and  $\mathbf{E} = 20 \, \text{V} \angle 0^\circ$

- d. The phasor diagram appears in Fig. 15.48.

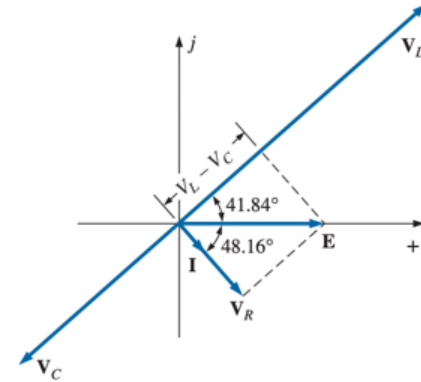

**FIG. 15.48**

Phasor diagram for the circuit in Fig. 15.46.

$$\begin{aligned} \text{f. } \mathbf{V}_R &= \frac{\mathbf{Z}_R \mathbf{E}}{\mathbf{Z}_T} = \frac{(10 \, \Omega \angle 0^\circ)(20 \, \text{V} \angle 0^\circ)}{15 \, \Omega \angle 48.16^\circ} = \frac{200 \, \text{V} \angle 0^\circ}{15 \angle 48.16^\circ} \\ &= \mathbf{13.3 \, \text{V} \angle -48.16^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{V}_C &= \frac{\mathbf{Z}_C \mathbf{E}}{\mathbf{Z}_T} = \frac{(26.5 \, \Omega \angle -90^\circ)(20 \, \text{V} \angle 0^\circ)}{15 \, \Omega \angle 48.16^\circ} = \frac{530.6 \, \text{V} \angle -90^\circ}{15 \angle 48.16^\circ} \\ &= \mathbf{35.37 \, \text{V} \angle -138.16^\circ} \end{aligned}$$

# Thank You

