

# Introduction to Electrical Circuits

## Mid Term Lecture – 7

Faculty Name: Rethwan Faiz  
Email ID: rethwan\_faiz@aiub.edu

### Reference Book:

### Introductory Circuit Analysis

Robert L. Boylestad, 11<sup>th</sup> Edition



# CONTENT



Week No.	Class No.	Chapter No.	Article No., Name and Contents	Example No.	Exercise No.
W4	MC7	Chapter 9	9.2 SUPERPOSITION THEOREM	See the circuit given	1,2,3,4
			9.3 THÉVENIN'S THEOREM	Try Exercise.	6, 7, 8, 9, 10, 13, 14, 15,



# SUPERPOSITION THEOREM

Find the solution to networks with two or more sources that are not in series or parallel.

Does not require the use of a mathematical technique such as determinants to find the required voltages or currents.

*The superposition theorem states the following:*

*The current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produced independently by each source.*

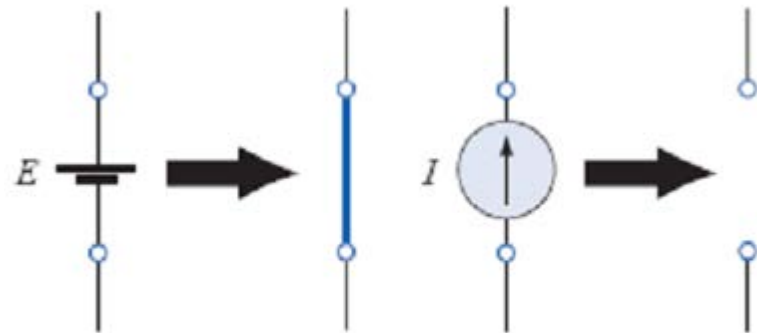


FIG. 9.1 Removing the effects of ideal sources.



# CHAPTER 9


## 9.2 SUPERPOSITION THEOREM

**EXAMPLE 9.5** Find the current through the  $2\ \Omega$  resistor of the network in Fig. 9.18. The presence of three sources results in three different networks to be analyzed.

**Solution:** Step 1:

Considering the effect of the  $12\text{ V}$  source (Fig. 9.19):

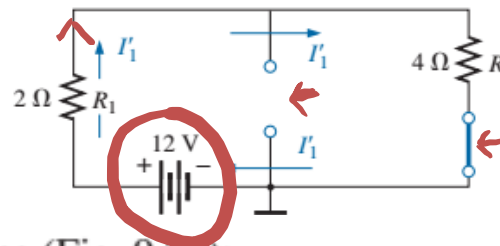
$$I'_1 = \frac{E_1}{R_1 + R_2} = \frac{12\text{ V}}{2\ \Omega + 4\ \Omega} = \frac{12\text{ V}}{6\ \Omega} = 2\text{ A}$$



Step 2:

Considering the effect of the  $6\text{ V}$  source (Fig. 9.20):
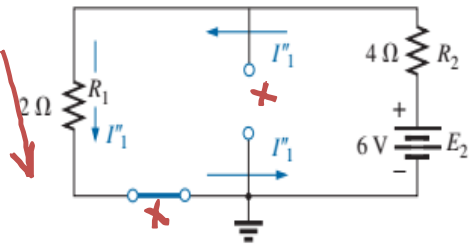
$$I''_1 = \frac{E_2}{R_1 + R_2} = \frac{6\text{ V}}{2\ \Omega + 4\ \Omega} = \frac{6\text{ V}}{6\ \Omega} = 1\text{ A}$$





Step 4:

The total current through the  $2\ \Omega$  resistor appears in Fig. 9.22 and

Step 3:

$$I'''_1 = \frac{R_2 I}{R_1 + R_2} = \frac{(4\ \Omega)(3\text{ A})}{2\ \Omega + 4\ \Omega} = \frac{12\text{ A}}{6} = 2\text{ A}$$
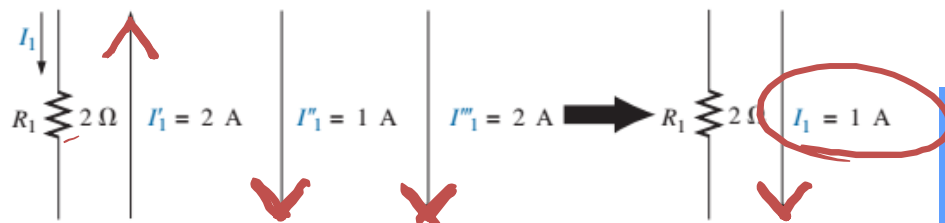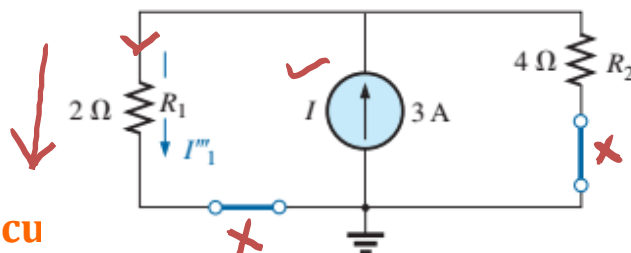
$$I_1 = \overbrace{I''_1 + I'''_1}^{\text{Same direction as } I_1 \text{ in Fig. 9.18}} - \overbrace{I'_1}^{\text{Opposite direction to } I_1 \text{ in Fig. 9.18}} = 1\text{ A} + 2\text{ A} - 2\text{ A} = 1\text{ A}$$



Facu

American International University-Bang

**EXAMPLE 9.2** Using the superposition theorem, determine the current through the  $12\ \Omega$  resistor in Fig. 9.5. Note that this is a two-source network of the type examined in the previous chapter when we applied branch-current analysis and mesh analysis.

**Solution:**



**Step 1:**

Considering the effects of the  $54\text{ V}$  source requires replacing the  $48\text{ V}$  source by a short-circuit equivalent.

$$R_T = R_1 + R_2 \parallel R_3 = 24\ \Omega + 12\ \Omega \parallel 4\ \Omega = 24\ \Omega + 3\ \Omega = 27\ \Omega$$

$$I_s = \frac{E_1}{R_T} = \frac{54\text{ V}}{27\ \Omega} = 2\text{ A}$$
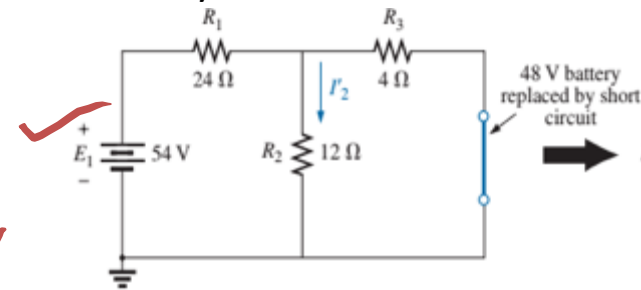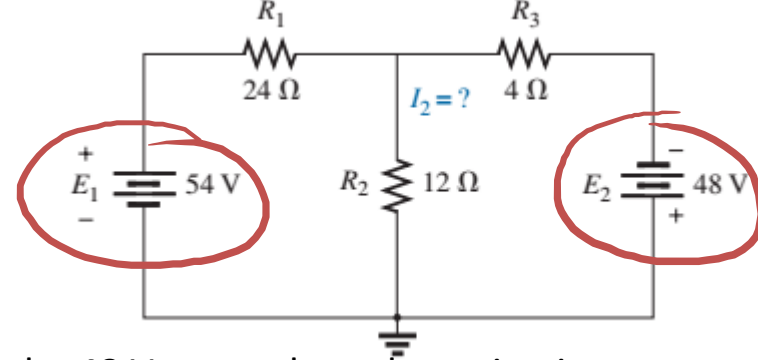
$$I'_2 = \frac{R_3 I_s}{R_3 + R_2} = \frac{(4\ \Omega)(2\text{ A})}{4\ \Omega + 12\ \Omega} = 0.5\text{ A}$$



**Step 2:**

If we now replace the  $54\text{ V}$  source by a short-circuit equivalent, the network in Fig. 9.7 results.



$$R_T = R_3 + R_2 \parallel R_1 = 4\ \Omega + 12\ \Omega \parallel 24\ \Omega = 4\ \Omega + 8\ \Omega = 12\ \Omega$$

$$I_s = \frac{E_2}{R_T} = \frac{48\text{ V}}{12\ \Omega} = 4\text{ A}$$

$$I''_2 = \frac{R_1 I_s}{R_1 + R_2} = \frac{(24\ \Omega)(4\text{ A})}{24\ \Omega + 12\ \Omega} = 2.67\text{ A}$$

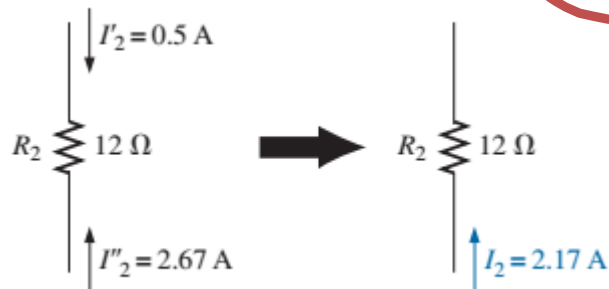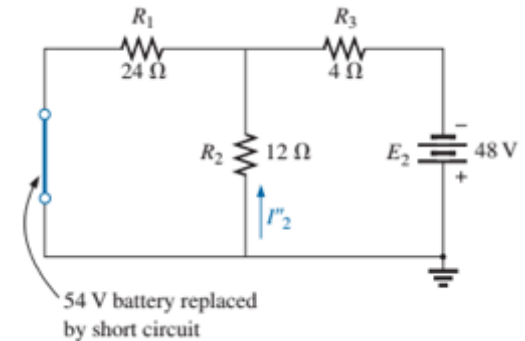**Step 3:**

$$I_2 = I''_2 - I'_2 = 2.67\text{ A} - 0.5\text{ A} = 2.17\text{ A}$$




Faculty

American International University Bangladesh

## 9.3 THÉVENIN'S THEOREM

*Any two-terminal dc network can be replaced by an equivalent circuit consisting solely of a voltage source and a series resistor as shown in the figure. This is called Thevenin Equivalent Circuit.*

*Thevenin equivalent circuit.*

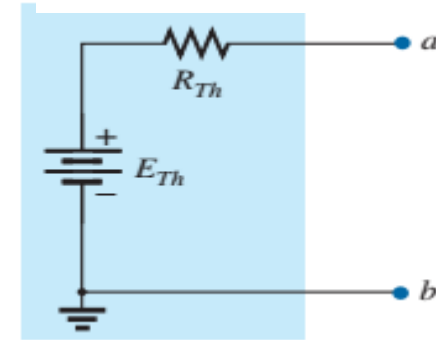

### Steps:

1. Remove that portion of the network where the Thévenin equivalent circuit is found. In this circuit the load resistor  $R_L$  be temporarily removed from the network. Marked the terminals (a and b) across which thevenin is going to be applied.

2. Calculate  $R_{Th}$  by first setting all sources to zero (voltage sources are replaced by short circuits, and current sources by open circuits).

3. Consider an imaginary current is entering through the marked terminal 'a'. Calculate  $R_{Th}$ .


4. Calculate  $E_{Th}$  by first returning all sources to their original position and finding the open-circuit voltage ( $V_{ab}$ ) between the marked terminals a and b.

5. Draw the Thévenin equivalent circuit.







**EXAMPLE 9.8** Find the Thévenin equivalent circuit for the network in the shaded area of the network in Fig. 9.37. Note in this example that there is no need for the section of the network to be preserved to be at the “end” of the configuration.

**Solution:**

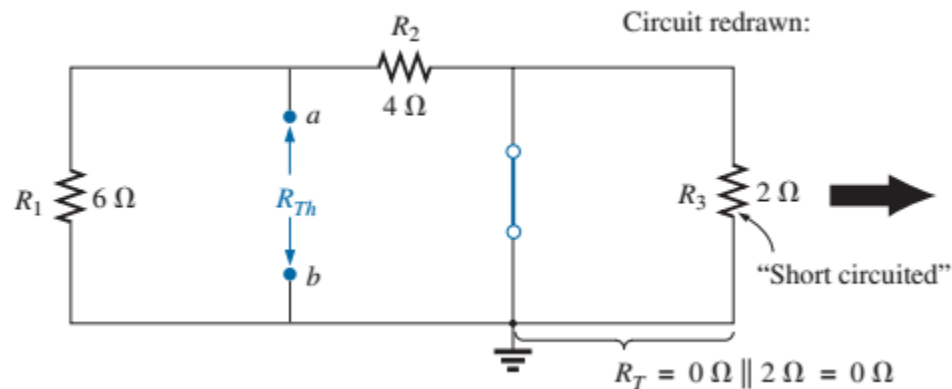

$$R_{Th} = R_1 \parallel R_2 = \frac{(6 \Omega)(4 \Omega)}{6 \Omega + 4 \Omega} = \frac{24 \Omega}{10} = 2.4 \Omega$$

Resultant Thevenin Equivalent Circuit:

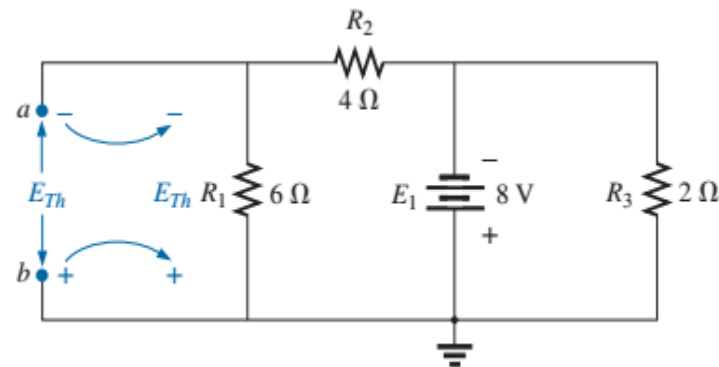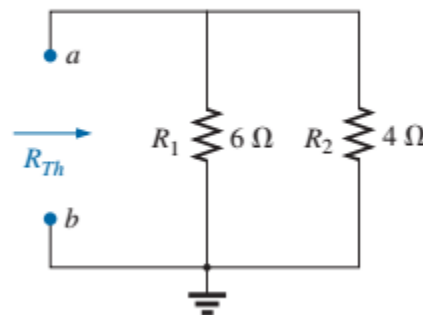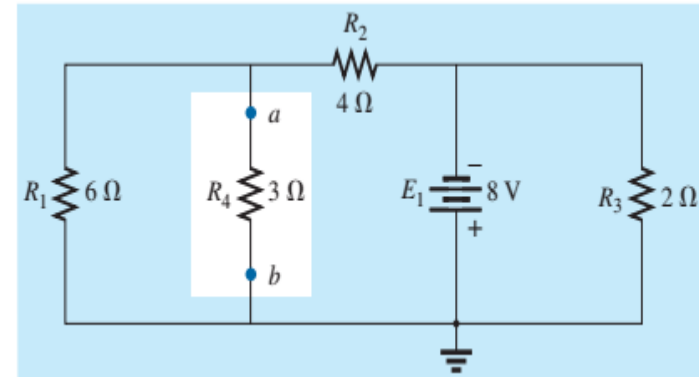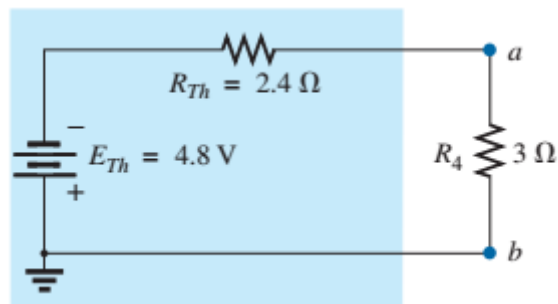


$$E_{Th} = \frac{R_1 E_1}{R_1 + R_2} = \frac{(6 \Omega)(8 \text{ V})}{6 \Omega + 4 \Omega} = \frac{48 \text{ V}}{10} = 4.8 \text{ V}$$





**EXAMPLE 9.9** Find the Thévenin equivalent circuit for the network in the shaded area of the bridge network in Fig. 9.43.

**Solution:**

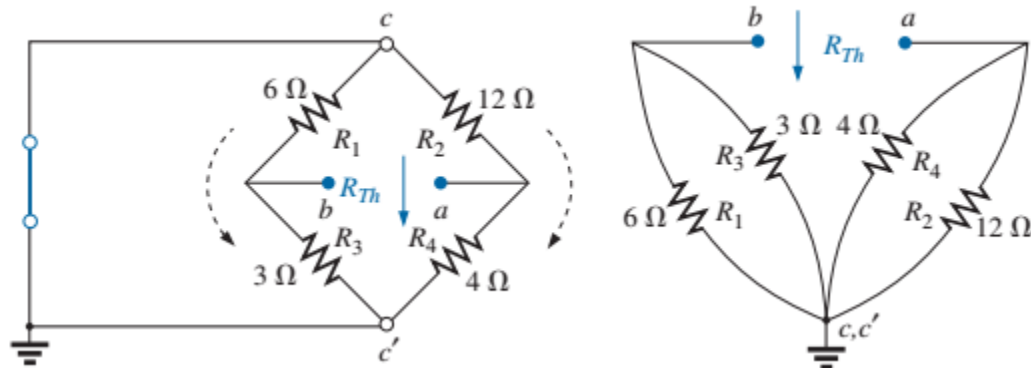

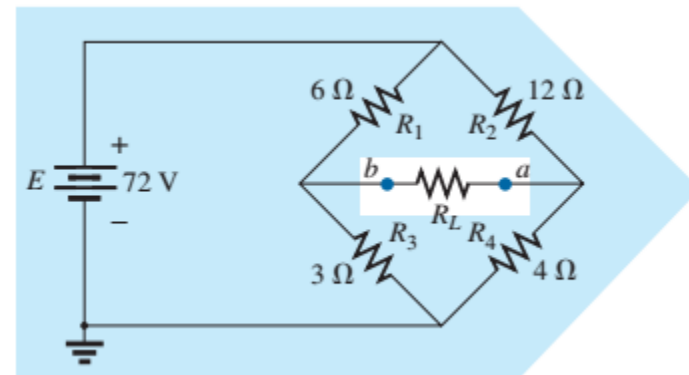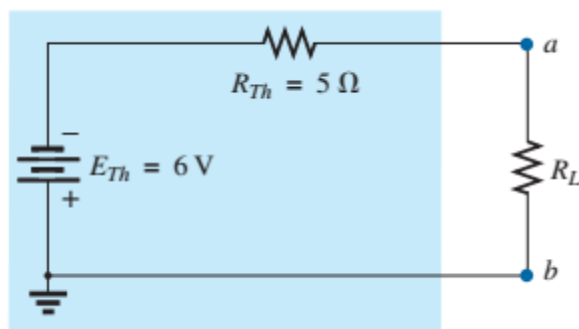
$$\begin{aligned} R_{Th} &= R_{a-b} = R_1 \parallel R_3 + R_2 \parallel R_4 \\ &= 6 \Omega \parallel 3 \Omega + 4 \Omega \parallel 12 \Omega \\ &= 2 \Omega + 3 \Omega = 5 \Omega \end{aligned}$$



$$V_1 = \frac{R_1 E}{R_1 + R_3} = \frac{(6 \Omega)(72 \text{ V})}{6 \Omega + 3 \Omega} = \frac{432 \text{ V}}{9} = 48 \text{ V}$$


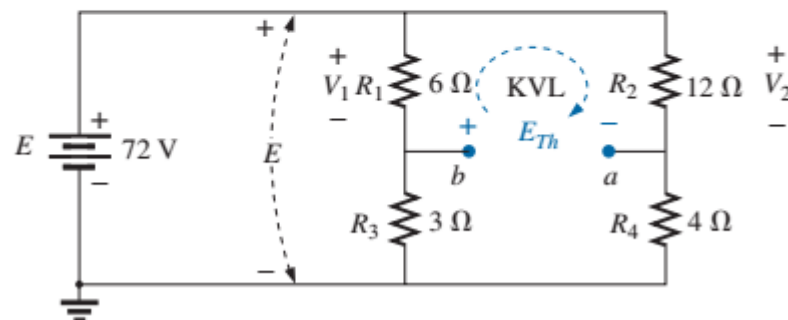
$$V_2 = \frac{R_2 E}{R_2 + R_4} = \frac{(12 \Omega)(72 \text{ V})}{12 \Omega + 4 \Omega} = \frac{864 \text{ V}}{16} = 54 \text{ V}$$



$$\begin{aligned} \Sigma_C V &= +E_{Th} + V_1 - V_2 = 0 \\ E_{Th} &= V_2 - V_1 = 54 \text{ V} - 48 \text{ V} = 6 \text{ V} \end{aligned}$$





# Class Practice

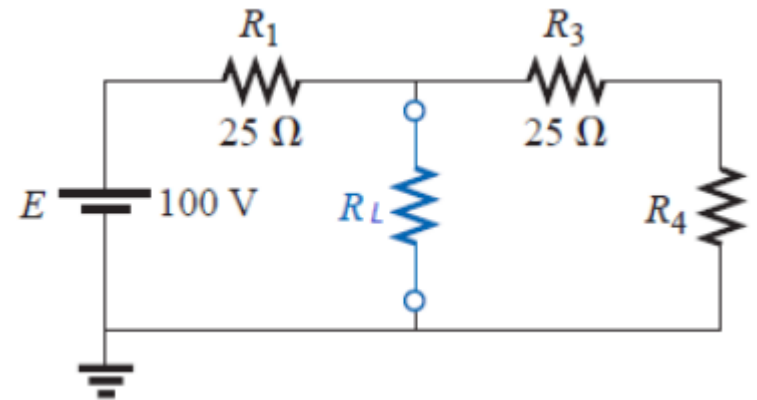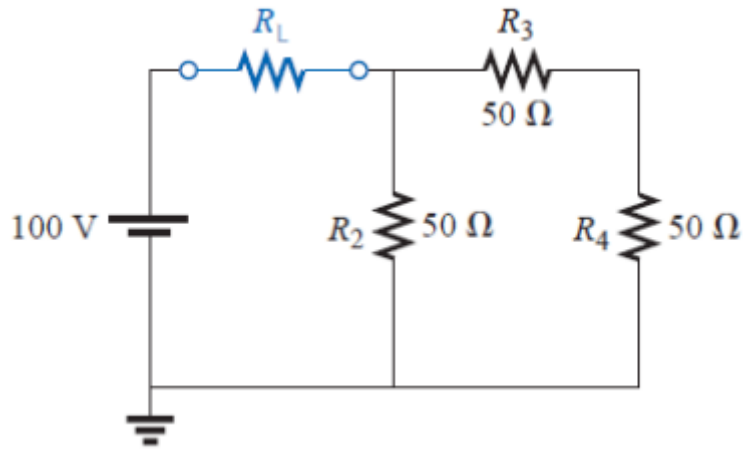

1. a. Using superposition, find the current through each resistor of the network in Fig. 9.119.
- b. Find the power delivered to  $R_1$  for each source.
- c. Find the power delivered to  $R_1$  using the total current through  $R_1$ .
- d. Does superposition apply to power effects? Explain.

### Solution:

a.  $E_1$ :

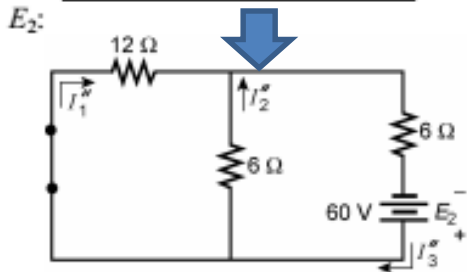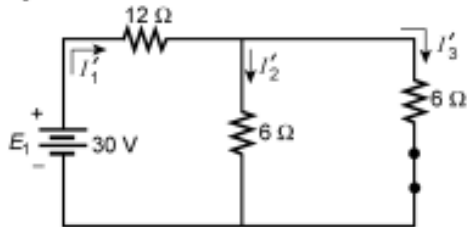

$$I_1' = \frac{30 \text{ V}}{12 \Omega + 6 \Omega \parallel 6 \Omega}$$

$$= \frac{30 \text{ V}}{12 \Omega + 3 \Omega} = 2 \text{ A}$$

$$I_2' = I_3' = \frac{I_1'}{2} = 1 \text{ A}$$

$$I_3'' = \frac{60 \text{ V}}{6 \Omega + 6 \Omega \parallel 12 \Omega} = \frac{60 \text{ V}}{6 \Omega + 4 \Omega}$$

$$= 6 \text{ A}$$

$$I_1'' = \frac{6 \Omega (I_3'')}{6 \Omega + 12 \Omega} = 2 \text{ A}$$

$$I_2'' = \frac{12 \Omega (I_3'')}{12 \Omega + 6 \Omega} = 4 \text{ A}$$

$$I_1 = I_1' + I_1'' = 2 \text{ A} + 2 \text{ A} = 4 \text{ A (dir. of } I_1')$$

$$I_2 = I_2'' - I_2' = 4 \text{ A} - 1 \text{ A} = 3 \text{ A (dir. of } I_2'')$$

$$I_3 = I_3' + I_3'' = 1 \text{ A} + 6 \text{ A} = 7 \text{ A (dir. of } I_3')$$


b.  $E_1$ :  $P_1' = I_1'^2 R_1 = (2 \text{ A})^2 12 \Omega = 48 \text{ W}$

$E_2$ :  $P_1'' = I_1''^2 R_1 = (2 \text{ A})^2 12 \Omega = 48 \text{ W}$

c.  $P_1 = I_1^2 R_1 = (4 \text{ A})^2 12 \Omega = 192 \text{ W}$


d.  $P_1' + P_1'' = 48 \text{ W} + 48 \text{ W} = 96 \text{ W} \neq 192 \text{ W} = P_1$

# Exercise Problems

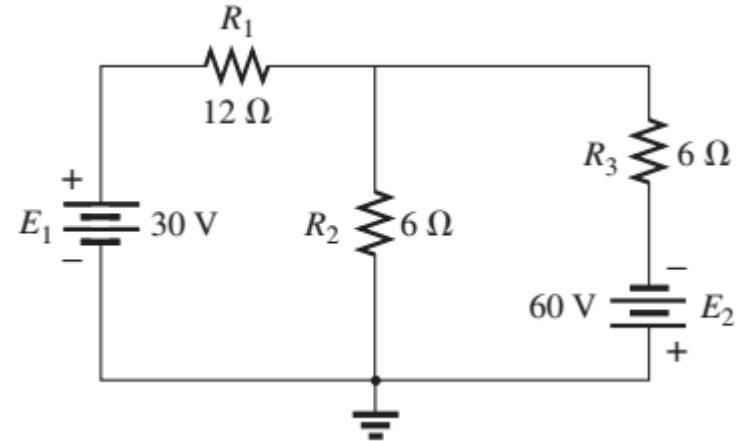


2. Using superposition, find the current  $I$  through the  $10\ \Omega$  resistor for the network in Fig. 9.120.

**Solution:**

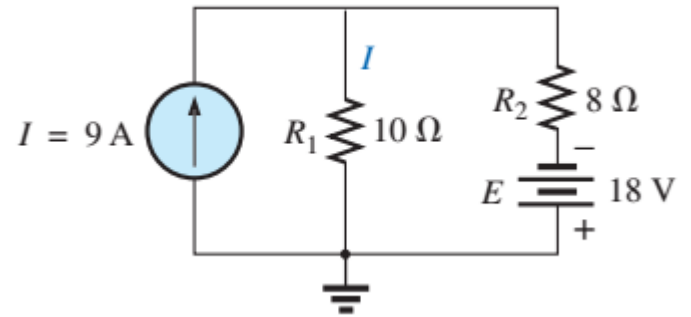


$I$ :

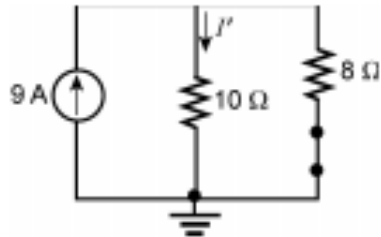


$$I' = \frac{8\ \Omega(9\ \text{A})}{8\ \Omega + 10\ \Omega} = 4\ \text{A}$$

$E$ :

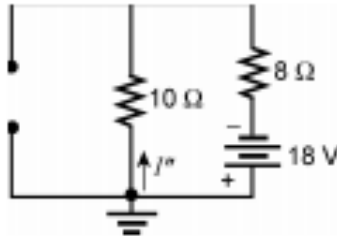

$$I'' = \frac{18\ \text{V}}{10\ \Omega + 8\ \Omega} = 1\ \text{A}$$

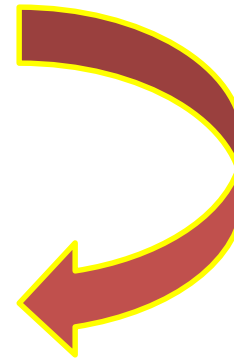
$$I = I' - I'' = 4\ \text{A} - 1\ \text{A} = 3\ \text{A (dir of } I')$$



3. Using superposition, find the current  $I$  through the 24 V source in Fig. 9.121.

**Solution:**


$E_1$ :

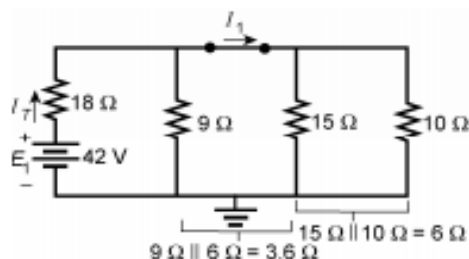

$$I_T = \frac{42 \text{ V}}{18 \Omega + 3.6 \Omega} = 1.944 \text{ A}$$

$$I_1 = \frac{9 \Omega (I_T)}{9 \Omega + 6 \Omega} = \frac{9 \Omega (1.944 \text{ A})}{15 \Omega} = 1.17 \text{ A}$$


$E_2$ :

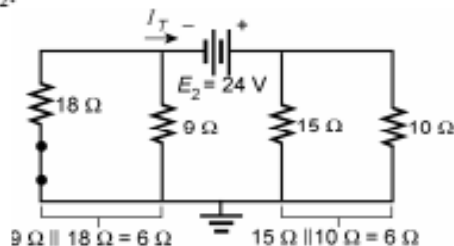


$$I_T = \frac{E_2}{R_T} = \frac{24 \text{ V}}{12 \Omega} = 2 \text{ A}$$

$$I_{24\text{V}} = I_T + I_1 = 2 \text{ A} + 1.17 \text{ A} = 3.17 \text{ A (dir. of } I_1)$$


$$E_1 = +42 \text{ V}$$

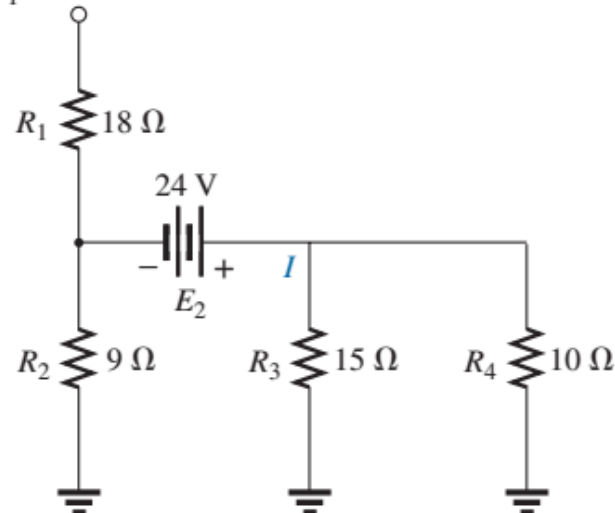

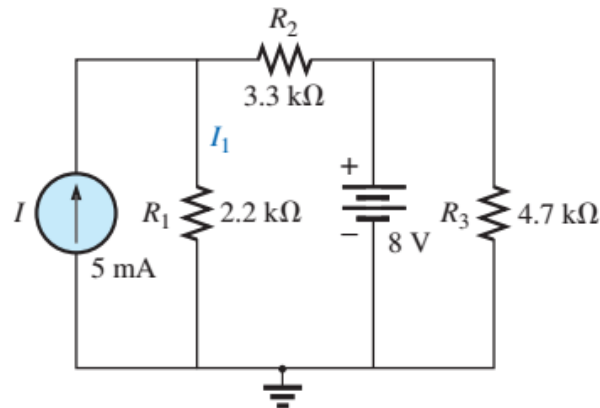
- \*4. Using superposition, find the current through  $R_1$  for the network in Fig. 9.122.



**Solution:**

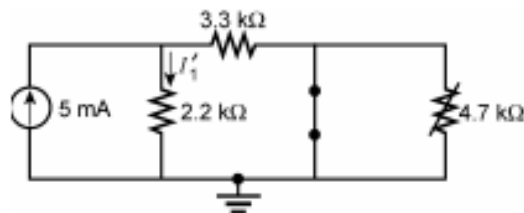
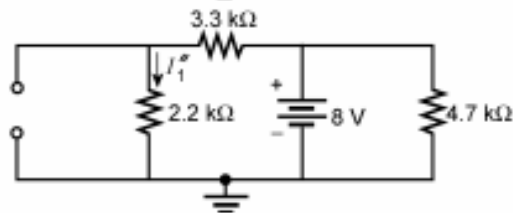
$$I'_1 = \frac{3.3 \text{ k}\Omega (5 \text{ mA})}{2.2 \text{ k}\Omega + 3.3 \text{ k}\Omega} = \frac{16.5 \text{ mA}}{5.5} = 3 \text{ mA}$$




$$I''_1 = \frac{8 \text{ V}}{3.3 \text{ k}\Omega + 2.2 \text{ k}\Omega} = \frac{8 \text{ V}}{5.5 \text{ k}\Omega} = 1.45 \text{ mA}$$

$$I_1 = I'_1 + I''_1 = 3 \text{ mA} + 1.45 \text{ mA} = 4.45 \text{ mA}$$



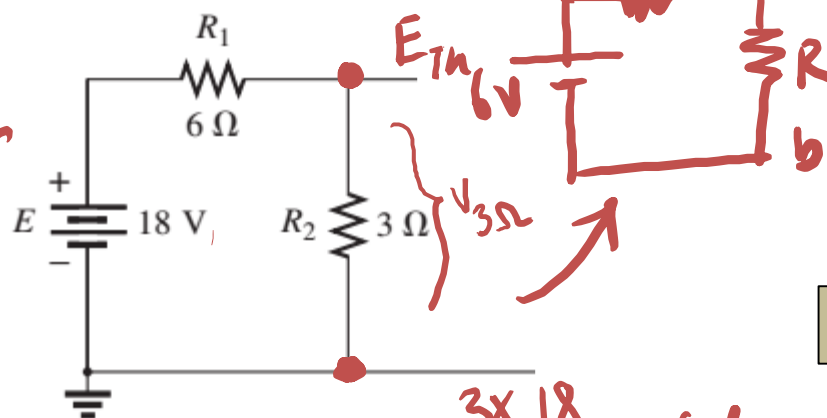7. a. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  in Fig. 9.125.  
b. Find the current through  $R$  when  $R$  is  $2\ \Omega$ ,  $30\ \Omega$ , and  $100\ \Omega$ .



**Solution:**

a.  $R_{Th} = R_3 + R_1 \parallel R_2 = 4\ \Omega + 6\ \Omega \parallel 3\ \Omega = 4\ \Omega + 2\ \Omega = 6\ \Omega$


$$E_{Th} = \frac{R_2 E}{R_2 + R_1} = \frac{3\ \Omega (18\ \text{V})}{3\ \Omega + 6\ \Omega} = 6\ \text{V}$$

b.  $I_1 = \frac{E_{Th}}{R_{Th} + R} = \frac{6\ \text{V}}{6\ \Omega + 2\ \Omega} = 0.75\ \text{A}$


$$I_2 = \frac{6\ \text{V}}{6\ \Omega + 30\ \Omega} = 166.67\ \text{mA}$$

$$I_3 = \frac{6\ \text{V}}{6\ \Omega + 100\ \Omega} = 56.60\ \text{mA}$$

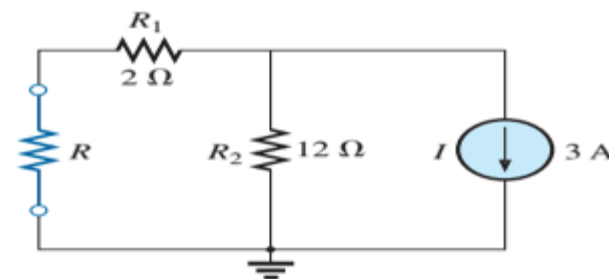
8. a. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  for the network in Fig. 9.126.  
b. Find the power delivered to  $R$  when  $R$  is  $2\ \Omega$  and  $100\ \Omega$ .



**Solution:**

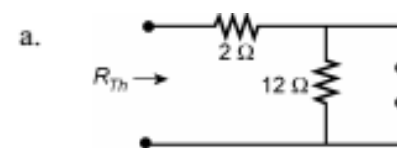
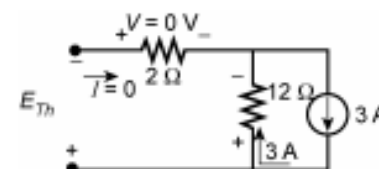
$$R_{Th} = 2\ \Omega + 12\ \Omega = 14\ \Omega$$




$$E_{Th} = IR = (3\ \text{A})(12\ \Omega) = 36\ \text{V}$$

b.  $R = 2\ \Omega: P = \left( \frac{E_{Th}}{R_{Th} + R} \right)^2 R = \left( \frac{36\ \text{V}}{14\ \Omega + 2\ \Omega} \right)^2 2\ \Omega = 10.13\ \text{W}$



$$R = 100\ \Omega: P = \left( \frac{36\ \text{V}}{14\ \Omega + 100\ \Omega} \right)^2 100\ \Omega = 9.97\ \text{W}$$



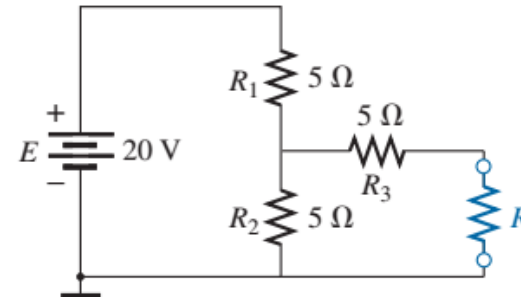9. a. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  for the network in Fig. 9.127.
- b. Find the power delivered to  $R$  when  $R$  is  $2\ \Omega$  and  $100\ \Omega$ .



**Solution:**

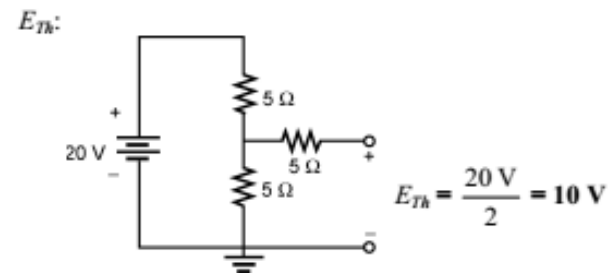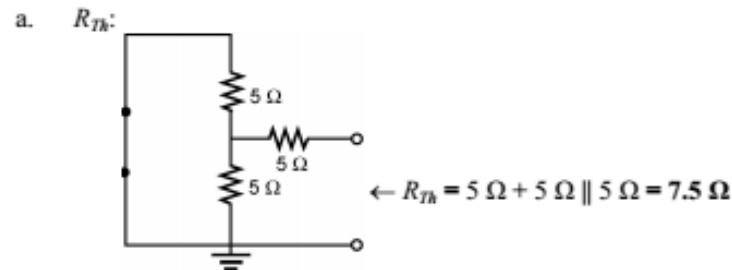



b.  $R = 2\ \Omega$ :  $P = \left( \frac{E_{Th}}{R_{Th} + R} \right)^2 R = \left( \frac{10\ \text{V}}{7.5\ \Omega + 2\ \Omega} \right)^2 2\ \Omega = 2.22\ \text{W}$

$R = 100\ \Omega$ :  $P = \left( \frac{10\ \text{V}}{7.5\ \Omega + 100\ \Omega} \right)^2 100\ \Omega = 0.87\ \text{W}$




10. Find the Thévenin equivalent circuit for the network external to the resistor  $R$  for the network in Fig. 9.128.

**Solution:**

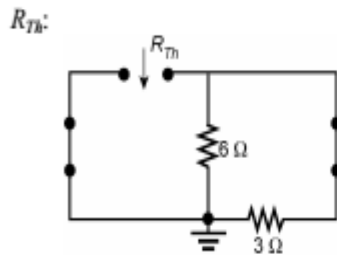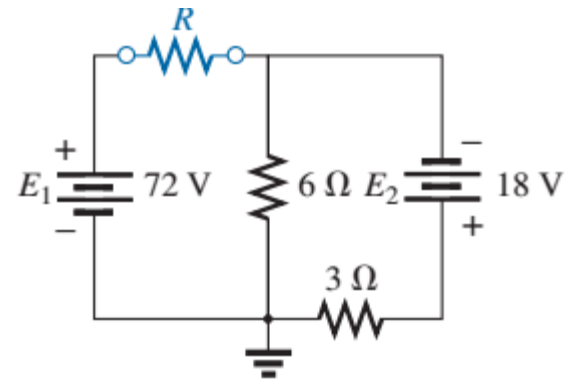
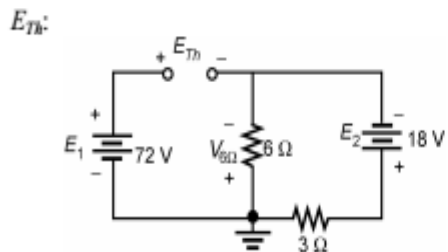
$$R_{Th} = 6\ \Omega \parallel 3\ \Omega = 2\ \Omega$$




$$V_{6\Omega} = \frac{6\ \Omega (18\ \text{V})}{6\ \Omega + 3\ \Omega} = 12\ \text{V}$$

$$E_{Th} = 72\ \text{V} + 12\ \text{V} = 84\ \text{V}$$






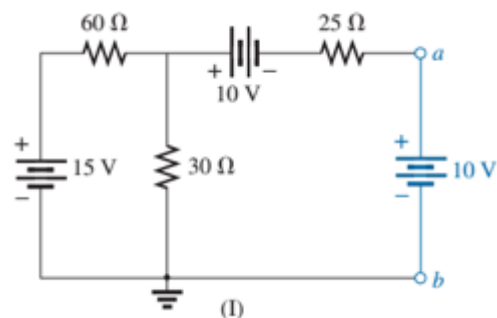\*13. Find the Thévenin equivalent circuit for the portions of the networks in Fig. 9.131 external to points  $a$  and  $b$ .




**Solution:**

(I):  $R_{Th}$ :

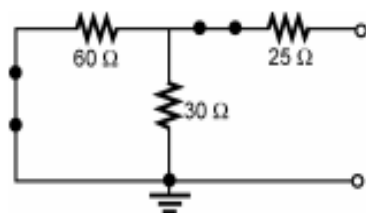


$$\leftarrow R_{Th} = 25 \Omega + 60 \Omega \parallel 30 \Omega = 45 \Omega$$


$E_{Th}$ :

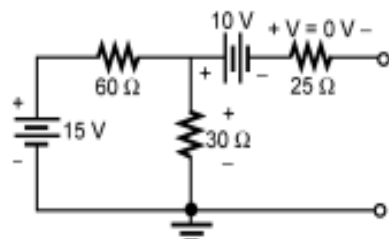
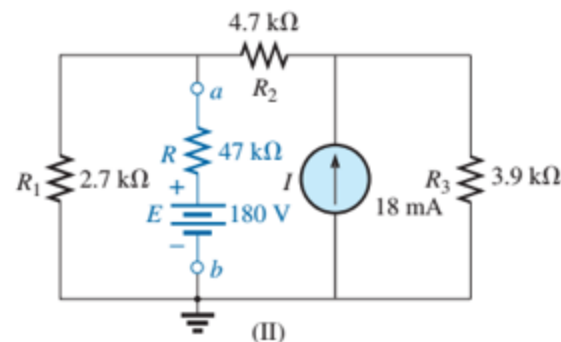
$$\begin{aligned} E_{Th} &= V_{30\Omega} - 10 \text{ V} - 0 \\ &= \frac{30 \Omega (15 \text{ V})}{30 \Omega + 60 \Omega} - 10 \text{ V} \\ &= 5 \text{ V} - 10 \text{ V} = -5 \text{ V} \end{aligned}$$




(II):  $R_{Th}$ :

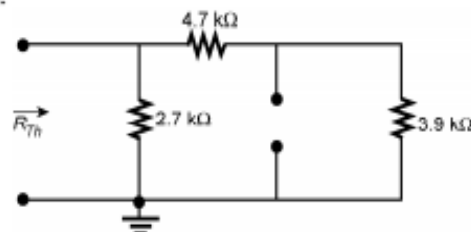

$$R_{Th} = 2.7 \text{ k}\Omega \parallel (4.7 \text{ k}\Omega + 3.9 \text{ k}\Omega) = 2.7 \text{ k}\Omega \parallel 8.6 \text{ k}\Omega = 2.06 \text{ k}\Omega$$

$E_{Th}$ :

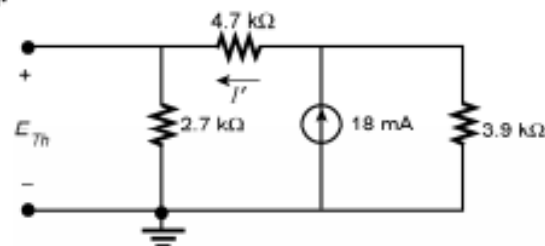


$$I' = \frac{3.9 \text{ k}\Omega (18 \text{ mA})}{3.9 \text{ k}\Omega + 7.4 \text{ k}\Omega} = 6.21 \text{ mA}$$

$$E_{Th} = I' (2.7 \text{ k}\Omega) = (6.21 \text{ mA})(2.7 \text{ k}\Omega) = 16.77 \text{ V}$$




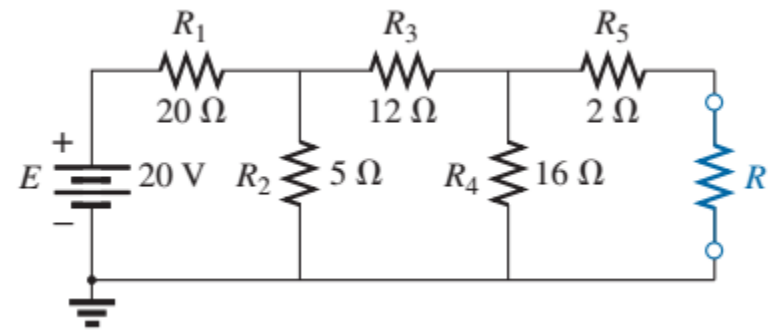- \*14. Determine the Thévenin equivalent circuit for the network external to the resistor  $R$  in both networks in Fig. 9.132.




**Solution:**

(I):  $R_{Th}$ :

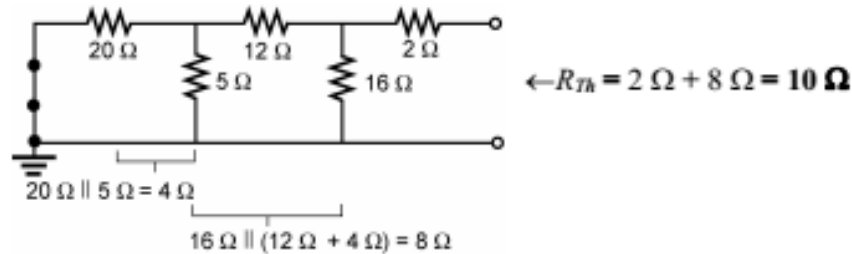

$E_{Th}$ :

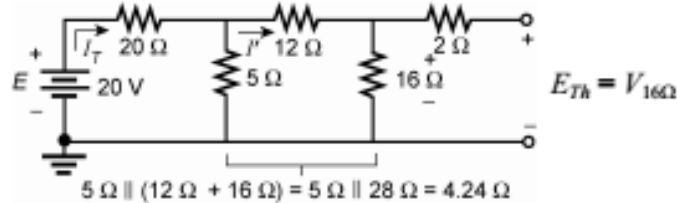

$$I_T = \frac{20\text{ V}}{20\Omega + 4.24\Omega} = 825.08\text{ mA}$$


$$I' = \frac{5\Omega(I_T)}{5\Omega + 28\Omega} = \frac{5\Omega(825.08\text{ mA})}{33\Omega} = 125.01\text{ mA}$$

$$E_{Th} = V_{16\Omega} = (I')(16\Omega) = (125.01\text{ mA})(16\Omega) = 2\text{ V}$$



- \*15. For the network in Fig. 9.133, find the Thévenin equivalent circuit for the network external to the load resistor  $R_L$ .

### Solution:

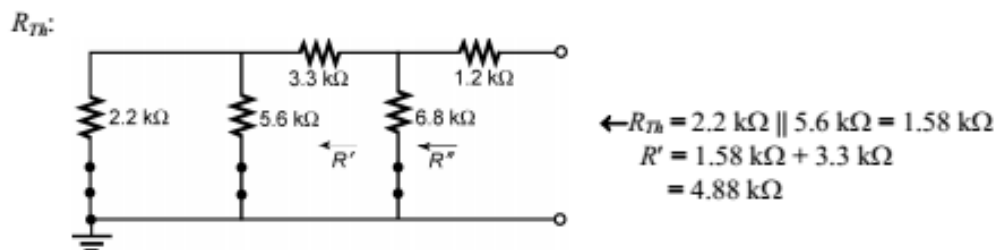

$$R'' = 4.88 \text{ k}\Omega \parallel 6.8 \text{ k}\Omega = 2.84 \text{ k}\Omega$$

$$R_{Th} = 1.2 \text{ k}\Omega + R'' = 1.2 \text{ k}\Omega + 2.84 \text{ k}\Omega = 4.04 \text{ k}\Omega$$


$E_{Th}$ : Source conversions:

$$I_1 = \frac{22 \text{ V}}{2.2 \text{ k}\Omega} = 10 \text{ mA}, R_s = 2.2 \text{ k}\Omega$$

$$I_2 = \frac{12 \text{ V}}{5.6 \text{ k}\Omega} = 2.14 \text{ mA}, R_s = 5.6 \text{ k}\Omega$$

Combining parallel current sources:  $I_T = I_1 - I_2 = 10 \text{ mA} - 2.14 \text{ mA} = 7.86 \text{ mA}$

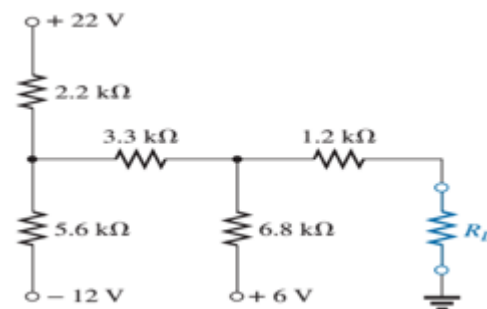
$$2.2 \text{ k}\Omega \parallel 5.6 \text{ k}\Omega = 1.58 \text{ k}\Omega$$



Source conversion:

$$E = (7.86 \text{ mA})(1.58 \text{ k}\Omega) = 12.42 \text{ V}$$
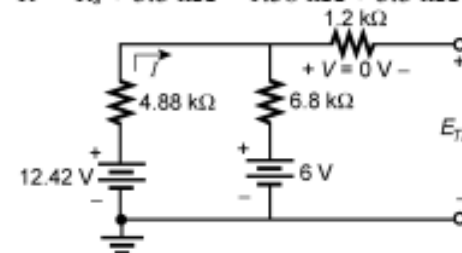
$$R' = R_s + 3.3 \text{ k}\Omega = 1.58 \text{ k}\Omega + 3.3 \text{ k}\Omega = 4.88 \text{ k}\Omega$$



$$I = \frac{12.42 \text{ V} - 6 \text{ V}}{4.88 \text{ k}\Omega + 6.8 \text{ k}\Omega} = \frac{6.42 \text{ V}}{11.68 \text{ k}\Omega} = 549.66 \mu\text{A}$$

$$V_{6.8 \text{ k}\Omega} = I(6.8 \text{ k}\Omega) = (549.66 \mu\text{A})(6.8 \text{ k}\Omega) = 3.74 \text{ V}$$

$$E_{Th} = 6 \text{ V} + V_{6.8 \text{ k}\Omega} = 6 \text{ V} + 3.74 \text{ V} = 9.74 \text{ V}$$



