

Introduction to Electrical Circuits

Final Term
Lecture - 03

Reference Book:

Introductory Circuit Analysis

Robert L. Boylestad, 11th Edition



Faculty of Engineering

American International University-Bangladesh

Parallel Circuits



Admittance

The reciprocal of **impedance** is called **admittance**.

The unit of admittance is **Siemens** [S].

$$Y = \frac{1}{Z} = \frac{I}{V} = Y \angle \theta_y = G + jB = g + jb = (\text{Conducacne}) + j(\text{Susceptance}) \text{ [S]}$$

$$\text{Conducacne : } G = g = Y \cos \theta_y \text{ [S]} \quad \text{Susceptance : } B = b = Y \sin \theta_y \text{ [S]}$$

G or g is called **conductance**. The unit of conductance is **mho** or **Siemens**.
Conductance (G or g) is the reciprocal of resistance (R).

B or b is called **susceptance**. The unit of susceptance is **Siemens**.
Susceptance (B or b) is the reciprocal of reactance (X).

$$G = g = \frac{1}{R} \text{ [S]} \quad B = b = \frac{1}{X} \text{ [S]} \quad B_L = b_L = \frac{1}{X_L} \text{ [S]} \quad B_C = b_C = \frac{1}{X_C} \text{ [S]}$$

B_L or b_L is called **inductive** susceptance.

B_C or b_C is called **capacitive** susceptance.



Admittance of a Resistance, Inductance and Capacitance

Admittance of a resistance: $Y_R = \frac{1}{Z_R} = \frac{1}{R\angle 0^\circ} = G\angle 0^\circ \text{ [S]}$

Admittance of an inductance: $Y_L = \frac{1}{Z_L} = \frac{1}{X_L\angle 90^\circ} = B_L\angle -90^\circ \text{ [S]}$

Admittance of a capacitance: $Y_C = \frac{1}{Z_C} = \frac{1}{X_C\angle -90^\circ} = B_C\angle 90^\circ \text{ [S]}$

Admittance of a *RL* series branch: $Y_{RL} = \frac{1}{Z_{RL}} = \frac{1}{R\angle 0^\circ + X_L\angle 90^\circ} = \frac{1}{R + jX_L} \text{ [S]}$

Admittance of a *RC* series branch: $Y_{RC} = \frac{1}{Z_{RC}} = \frac{1}{R\angle 0^\circ + X_C\angle -90^\circ} = \frac{1}{R - jX_C} \text{ [S]}$

Admittance of a *RLC* series branch:

$$Y_{RLC} = \frac{1}{Z_{RLC}} = \frac{1}{R\angle 0^\circ + X_L\angle 90^\circ + X_C\angle -90^\circ} = \frac{1}{R + jX_L - jX_C} \text{ [S]}$$



For ac parallel networks, the total admittance is simply the sum of the admittance levels of all the parallel branches.

$$\mathbf{Y}_T = \mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_3 + \cdots + \mathbf{Y}_N$$

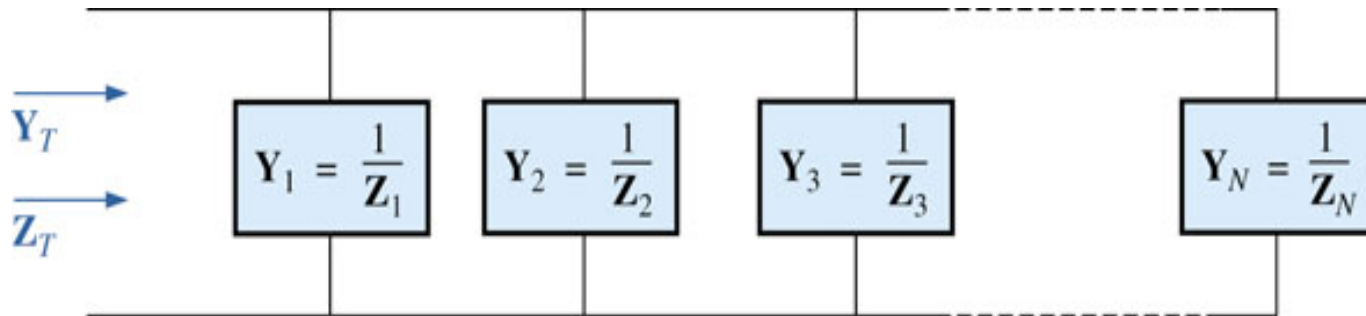


FIG. 15.58 Parallel ac network.

$$\mathbf{Y}_T = \frac{1}{\mathbf{Z}_T}$$

$$\frac{1}{\mathbf{Z}_T} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} + \cdots + \frac{1}{\mathbf{Z}_N}$$

For any configuration (series, parallel, series-parallel, and so on), the angle associated with the total admittance is the angle by which the source current leads the applied voltage. For inductive networks, θ_T is negative, whereas for capacitive networks, θ_T is positive.

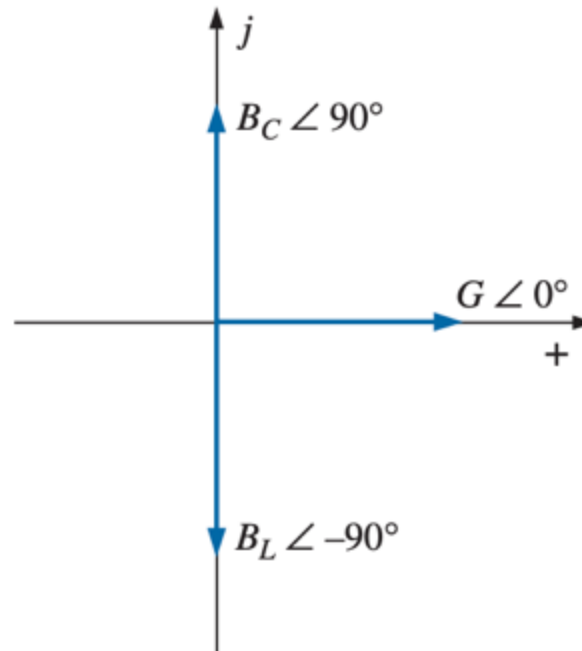


FIG. 16.8
Admittance diagram.



Example: For the parallel R - L network of Fig. 16.3:

- Determine the input impedance.
- Draw the impedance diagram.
- Find the admittance of each parallel element.
- Calculate the total admittance of the network.
- Sketch the admittance diagram.

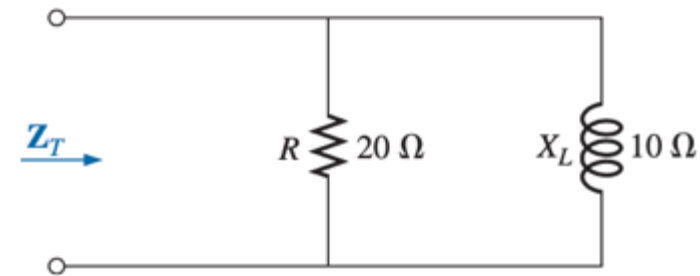


FIG. 16.3

Example 16.1.

Solutions:

$$\begin{aligned} \text{a. } Z_T &= \frac{Z_R Z_L}{Z_R + Z_L} = \frac{(20\ \Omega \angle 0^\circ)(10\ \Omega \angle 90^\circ)}{20\ \Omega + j10\ \Omega} \\ &= \frac{200\ \Omega \angle 90^\circ}{22.361 \angle 26.57^\circ} = \mathbf{8.93\ \Omega \angle 63.43^\circ} \\ &= \mathbf{4.00\ \Omega + j7.95\ \Omega = R_T + jX_L = 8.93\ \Omega \angle 63.43^\circ} \end{aligned}$$

- The impedance diagram appears in Fig. 16.4.

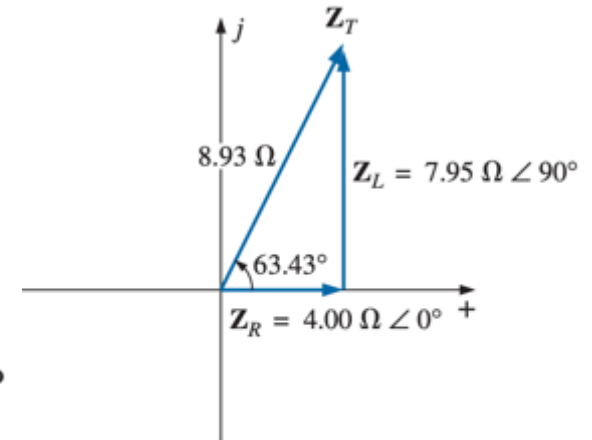


FIG. 16.4

Impedance diagram for the network in Fig. 16.3.



$$\begin{aligned} \text{c. } \mathbf{Y}_R &= G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{20 \, \Omega} \angle 0^\circ = \mathbf{0.05 \, S \angle 0^\circ} \\ &= \mathbf{0.05 \, S + j0} \end{aligned}$$

$$\begin{aligned} \mathbf{Y}_L &= B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{10 \, \Omega} \angle -90^\circ \\ &= \mathbf{0.1 \, S \angle -90^\circ = 0 - j0.1 \, S} \end{aligned}$$

$$\begin{aligned} \text{d. } \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L = (0.05 \, S + j0) + (0 - j0.1 \, S) \\ &= \mathbf{0.05 \, S - j0.1 \, S = G - jB_L = 0.112 \, S \angle -63.43^\circ} \end{aligned}$$

e. The admittance diagram appears in Fig. 16.9.

$$\begin{aligned} \mathbf{Z}_T &= \frac{1}{\mathbf{Y}_T} = \frac{1}{0.112 \, S \angle -63.43^\circ} \\ &= \mathbf{8.93 \, \Omega \angle 63.43^\circ} \text{—a perfect match} \end{aligned}$$

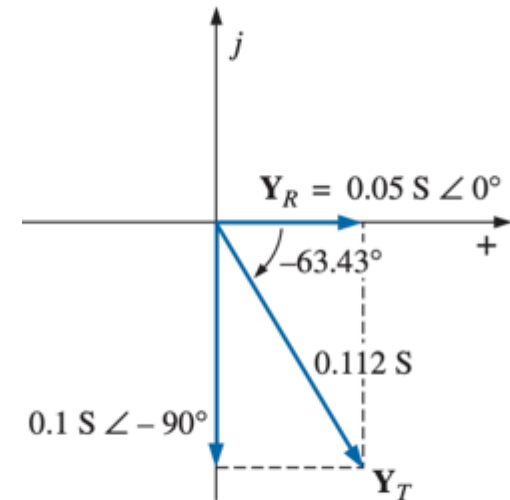


FIG. 16.9

Admittance diagram for the network in Fig. 16.3.



Example: For the network of Fig 16.5:

- Determine the total impedance.
- Sketch the impedance diagram.
- Find the admittance for each parallel branch.
- Calculate the total admittance of the network.
- Sketch the admittance diagram.

Solutions:

$$\begin{aligned} Z_T &= \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}} \\ &= \frac{1}{\frac{1}{5 \Omega \angle 0^\circ} + \frac{1}{8 \Omega \angle 90^\circ} + \frac{1}{20 \Omega \angle -90^\circ}} \\ &= \frac{1}{0.2 \text{ S} \angle 0^\circ + 0.125 \text{ S} \angle -90^\circ + 0.05 \text{ S} \angle 90^\circ} \\ &= \frac{1}{0.2 \text{ S} - j 0.075 \text{ S}} = \frac{1}{0.2136 \text{ S} \angle -20.56^\circ} \\ &= 4.68 \Omega \angle 20.56^\circ \end{aligned}$$


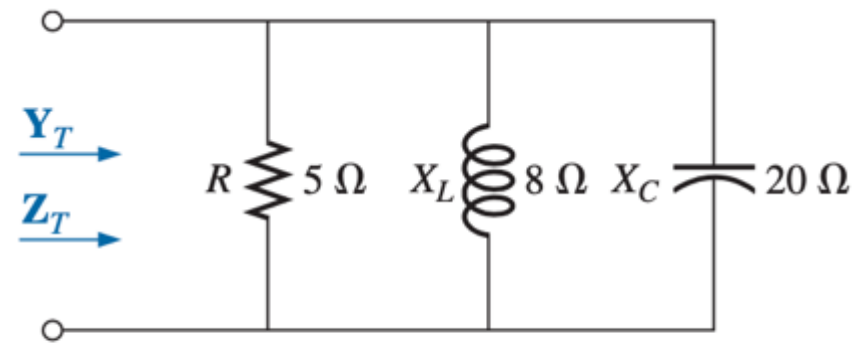


FIG. 16.5
Example 16.2.

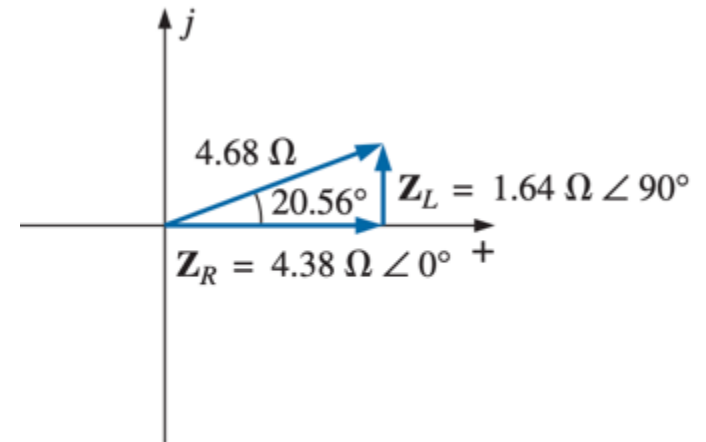

$$\begin{aligned}
 \mathbf{Z}_T &= \frac{\mathbf{Z}_R \mathbf{Z}_L \mathbf{Z}_C}{\mathbf{Z}_R \mathbf{Z}_L + \mathbf{Z}_L \mathbf{Z}_C + \mathbf{Z}_R \mathbf{Z}_C} \\
 &= \frac{(5 \Omega \angle 0^\circ)(8 \Omega \angle 90^\circ)(20 \Omega \angle -90^\circ)}{(5 \Omega \angle 0^\circ)(8 \Omega \angle 90^\circ) + (8 \Omega \angle 90^\circ)(20 \Omega \angle -90^\circ) + (5 \Omega \angle 0^\circ)(20 \Omega \angle -90^\circ)} \\
 &= \frac{800 \Omega \angle 0^\circ}{40 \angle 90^\circ + 160 \angle 0^\circ + 100 \angle -90^\circ} \\
 &= \frac{800 \Omega}{160 + j 40 - j 100} = \frac{800 \Omega}{160 - j 60} \\
 &= \frac{800 \Omega}{170.88 \angle -20.56^\circ} \\
 &= 4.68 \Omega \angle 20.56^\circ = 4.38 \Omega + j 1.64 \Omega
 \end{aligned}$$



b. The impedance diagram appears in Fig. 16.6.

FIG. 16.6

Impedance diagram for the network in Fig. 16.5.



$$\begin{aligned} \text{c. } \mathbf{Y}_R &= G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{5 \, \Omega} \angle 0^\circ \\ &= \mathbf{0.2 \, S \angle 0^\circ = 0.2 \, S + j0} \end{aligned}$$

$$\begin{aligned} \mathbf{Y}_L &= B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{8 \, \Omega} \angle -90^\circ \\ &= \mathbf{0.125 \, S \angle -90^\circ = 0 - j0.125 \, S} \end{aligned}$$

$$\begin{aligned} \mathbf{Y}_C &= B_C \angle 90^\circ = \frac{1}{X_C} \angle 90^\circ = \frac{1}{20 \, \Omega} \angle 90^\circ \\ &= \mathbf{0.05 \, S \angle +90^\circ = 0 + j0.05 \, S} \end{aligned}$$

$$\begin{aligned} \text{d. } \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L + \mathbf{Y}_C \\ &= (0.2 \, S + j0) + (0 - j0.125 \, S) + (0 + j0.05 \, S) \\ &= 0.2 \, S - j0.075 \, S = \mathbf{0.214 \, S \angle -20.56^\circ} \end{aligned}$$

e. The admittance diagram appears in Fig. 16.10.

$$\begin{aligned} \mathbf{Z}_T &= \frac{1}{\mathbf{Y}_T} = \frac{1}{0.214 \, S \angle -20.56^\circ} \\ &= \mathbf{4.68 \, \Omega \angle 20.56^\circ} \text{—a perfect match} \end{aligned}$$

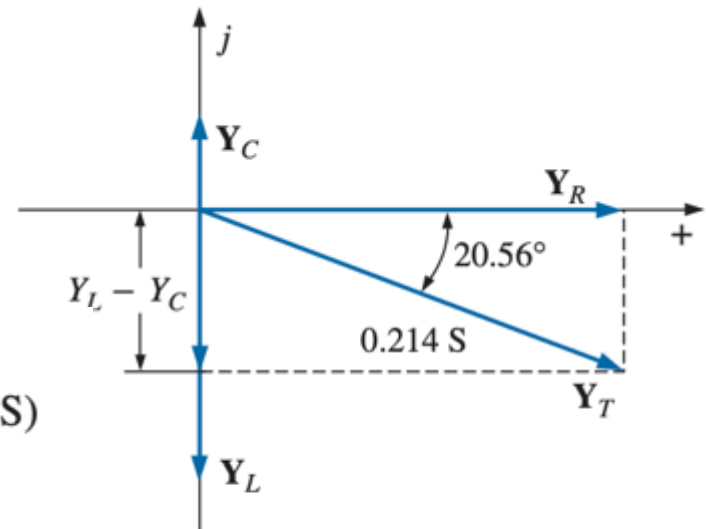


FIG. 16.10

Admittance diagram for the network in Fig. 16.5.



Example



Calculate the total admittance and current for the following circuit.

$$G = \frac{1}{3.33} = 0.3 \text{ [S]} \quad B_L = \frac{1}{2.5} = 0.4 \text{ [S]}$$

$$Y_R = 0.3 \angle 0^\circ = 0.3 \text{ [S]} \quad Y_L = 0.4 \angle -90^\circ = -j0.4 \text{ [S]}$$

$$Y = 0.3 \angle 0^\circ + 0.4 \angle -90^\circ = 0.3 - j0.4 = 0.5 \angle -53.13^\circ \text{ [S]}$$
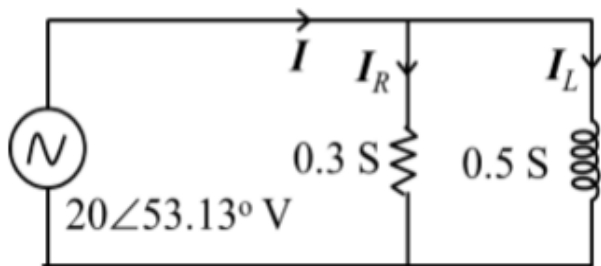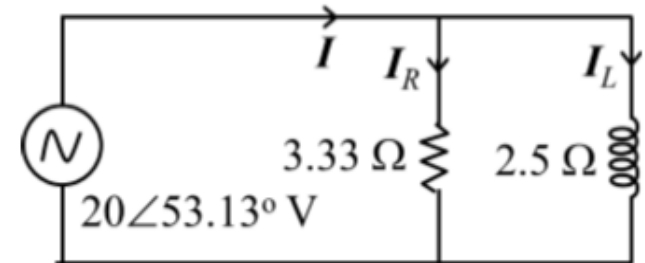
$$Z = \frac{1}{Y} = \frac{1}{0.5 \angle -53.13^\circ} = 2 \angle 53.13^\circ \text{ [\Omega]}$$



$$I = \frac{V}{Z} = YV = (0.5 \angle -53.13^\circ)(20 \angle 53.13^\circ) = 10 \angle 0^\circ \text{ [A]}$$

$$I_R = \frac{V}{Z_R} = Y_R V = (0.3 \angle 0^\circ)(20 \angle 53.13^\circ) = 6 \angle 53.13^\circ \text{ [A]}$$

$$I_L = \frac{V}{Z_L} = Y_L V = (0.4 \angle -90^\circ)(20 \angle 53.13^\circ) = 8 \angle -36.87^\circ \text{ [A]}$$



$$\theta = \theta_v - \theta_i = 53.13^\circ - 0^\circ = 53.13^\circ$$

$$pf = \cos(53.13^\circ) = 0.6 \text{ lagging}$$

$$rf = \sin(53.13^\circ) = 0.8$$



$$S = VI = 20 \times 10 = 200 \text{ VA}$$

$$P = VI \cos \theta = 20 \times 10 \times 0.6 = 120 \text{ W}$$


$$Q = VI \sin \theta = 20 \times 10 \times 0.8 = 160 \text{ VAR}$$

$$p(t) = 120(1 - \cos 2\omega t) + 160 \sin 2\omega t$$
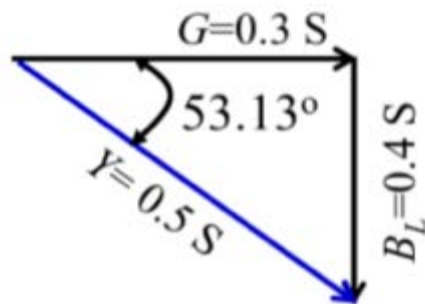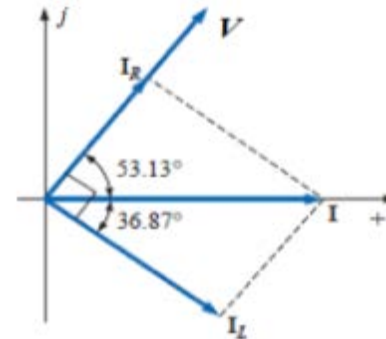
$$Q = I_L^2 X_L = 8^2 \times 2.5 = 160 \text{ VAR}$$



Admittance Diagram

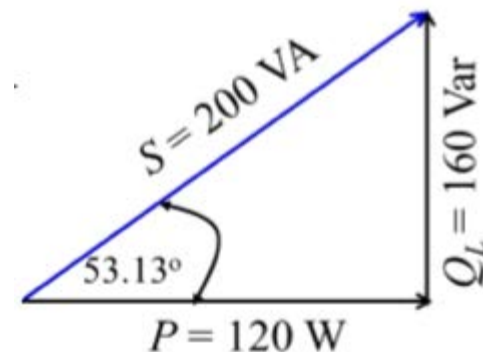

Power Triangle

Example



Calculate the total admittance and current for the following circuit.

$$G = \frac{1}{1.67} = 0.6 \text{ [S]} \quad B_C = \frac{1}{1.25} = 0.8 \text{ [S]}$$

$$Y_R = 0.6 \angle 0^\circ = 0.6 \text{ [S]} \quad Y_C = 0.8 \angle 90^\circ = j0.8 \text{ [S]}$$

$$Y = 0.6 \angle 0^\circ + 0.8 \angle 90^\circ = 0.6 + j0.8 = 1.0 \angle 53.13^\circ \text{ [S]}$$
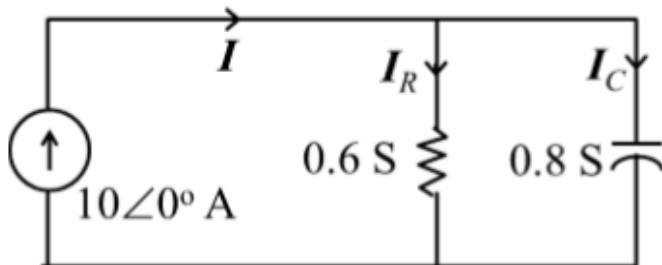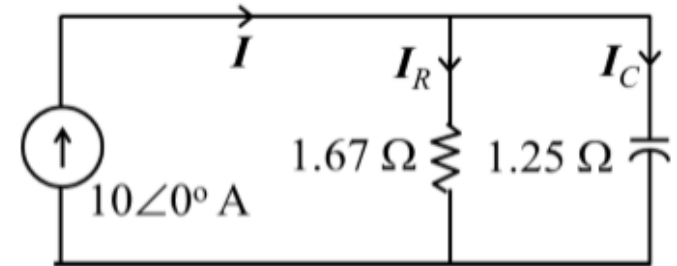
$$Z = \frac{1}{Y} = \frac{1}{1 \angle 53.13^\circ} = 1 \angle -53.13^\circ \text{ [\Omega]}$$



$$V = IZ = \frac{I}{Y} = \frac{10 \angle 0^\circ}{1 \angle 53.13^\circ} = 10 \angle -53.13^\circ \text{ [V]}$$

$$I_R = Y_R V = (0.6 \angle 0^\circ)(10 \angle -53.13^\circ) = 6 \angle -53.13^\circ \text{ [A]}$$

$$I_C = Y_C V = (0.8 \angle 90^\circ)(10 \angle -53.13^\circ) = 8 \angle 36.87^\circ \text{ [A]}$$



$$\theta = \theta_v - \theta_i = -53.13^\circ - 0^\circ = -53.13^\circ$$

$$pf = \cos(-53.13^\circ) = 0.6 \text{ leading}$$



$$rf = \sin(-53.13^\circ) = -0.8$$

$$Q = I_C^2 X_C = 8^2 \times 1.25 = 80 \text{ VAR}$$


$$S = VI = 10 \times 10 = 100 \text{ VA}$$

$$P = VI \cos \theta = 10 \times 10 \times 0.6 = 60 \text{ W}$$
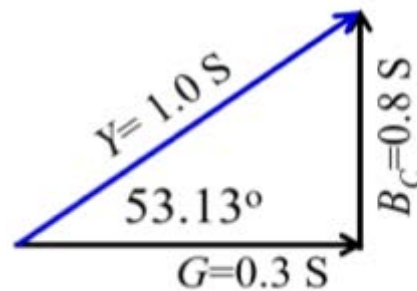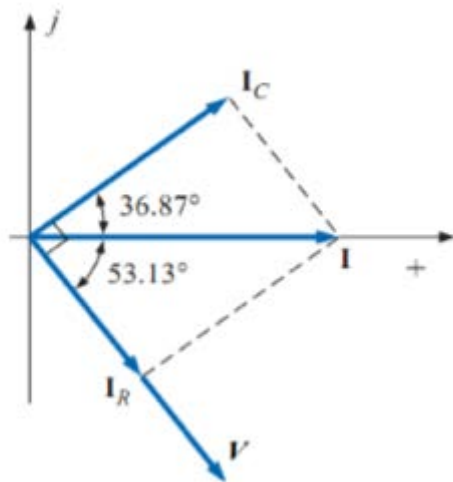
$$Q = VI \sin \theta = 10 \times 10 \times -0.8 = -80 \text{ VAR}$$



Admittance Diagram

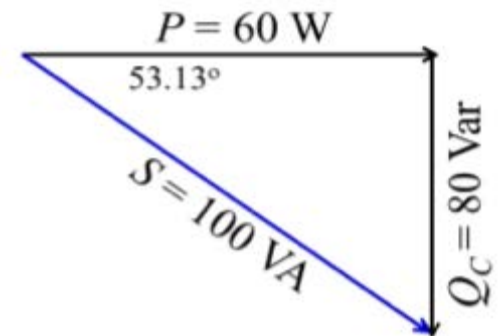

Power Triangle



Current Divider Rule

The current (I_x) flows one or more elements in parallel that have total admittance Y_x or impedance Z_x , can be given by:


$$I_x = \frac{Y_x}{Y_T} I = \frac{Z_T}{Z_x} I$$

where, I is the total current flows the parallel circuit, and Y_T is the total admittance of the parallel circuit.

Current Divider Rule only for two branch circuit:

$$I_1 = \frac{Y_1}{Y_T} I_T = \frac{Z_T}{Z_1} I_T = \frac{Z_2}{Z_1 + Z_2} I_T$$
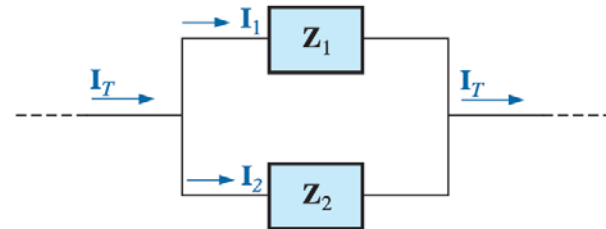
$$I_2 = \frac{Y_2}{Y_T} I_T = \frac{Z_T}{Z_2} I_T = \frac{Z_1}{Z_1 + Z_2} I_T$$



Example: Using the current divider rule, find the current through each impedance in Fig. 16.28.

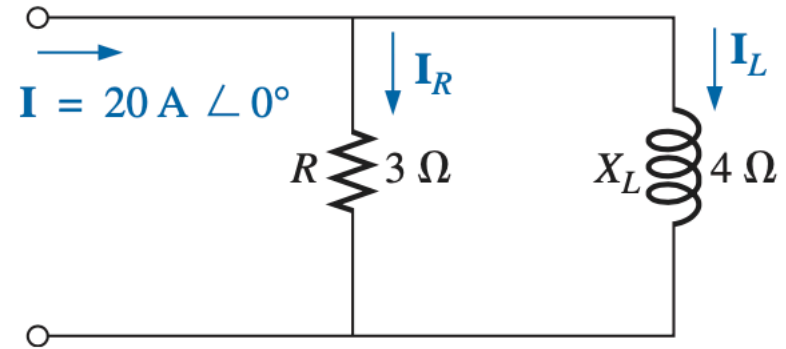


FIG. 16.28

Example 16.6.

Solution:

$$\begin{aligned} \mathbf{I}_R &= \frac{\mathbf{Z}_L \mathbf{I}_T}{\mathbf{Z}_R + \mathbf{Z}_L} = \frac{(4 \Omega \angle 90^\circ)(20 \text{ A } \angle 0^\circ)}{3 \Omega \angle 0^\circ + 4 \Omega \angle 90^\circ} = \frac{80 \text{ A } \angle 90^\circ}{5 \angle 53.13^\circ} \\ &= 16 \text{ A } \angle 36.87^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_L &= \frac{\mathbf{Z}_R \mathbf{I}_T}{\mathbf{Z}_R + \mathbf{Z}_L} = \frac{(3 \Omega \angle 0^\circ)(20 \text{ A } \angle 0^\circ)}{5 \angle 53.13^\circ} = \frac{60 \text{ A } \angle 0^\circ}{5 \angle 53.13^\circ} \\ &= 12 \text{ A } \angle -53.13^\circ \end{aligned}$$



Example: Using the current divider rule, find the current through each parallel branch in Fig. 16.29.

$$\mathbf{Z}_{RL} = 1 + j8 \, \Omega$$

$$\mathbf{Z}_C = -j2 = 2 \angle -90^\circ \, \Omega$$

Solution:

$$\begin{aligned} \mathbf{I}_{R-L} &= \frac{\mathbf{Z}_C \mathbf{I}_T}{\mathbf{Z}_C + \mathbf{Z}_{R-L}} = \frac{(2 \, \Omega \angle -90^\circ)(5 \, \text{A} \angle 30^\circ)}{-j2 \, \Omega + 1 \, \Omega + j8 \, \Omega} = \frac{10 \, \text{A} \angle -60^\circ}{1 + j6} \\ &= \frac{10 \, \text{A} \angle -60^\circ}{6.083 \angle 80.54^\circ} \cong \mathbf{1.64 \, \text{A} \angle -140.54^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_C &= \frac{\mathbf{Z}_{R-L} \mathbf{I}_T}{\mathbf{Z}_{R-L} + \mathbf{Z}_C} = \frac{(1 \, \Omega + j8 \, \Omega)(5 \, \text{A} \angle 30^\circ)}{6.08 \, \Omega \angle 80.54^\circ} \\ &= \frac{(8.06 \angle 82.87^\circ)(5 \, \text{A} \angle 30^\circ)}{6.08 \angle 80.54^\circ} = \frac{40.30 \, \text{A} \angle 112.87^\circ}{6.083 \angle 80.54^\circ} \\ &= \mathbf{6.63 \, \text{A} \angle 32.33^\circ} \end{aligned}$$

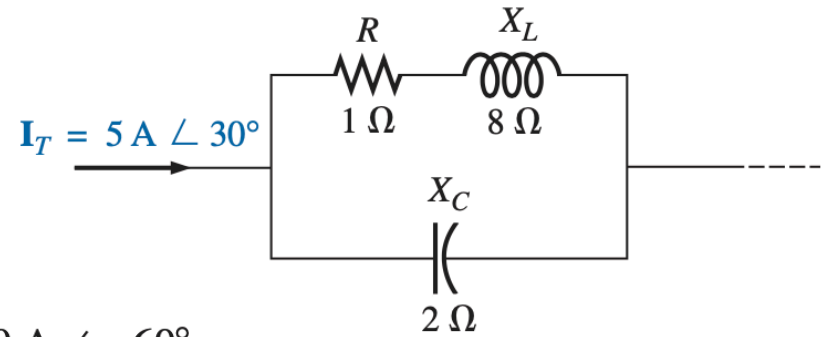


FIG. 16.29
Example 16.7.



Thank You

